

**PART I. SOLUTIONS TO PROBLEM SETS**

2.1  $v = \sqrt{2} \times 120 \cos(\omega t + 30^\circ) \Rightarrow V = 120 \angle 30^\circ \text{ V}$   
 $i = \sqrt{2} \times 10 \cos(\omega t - 30^\circ) \Rightarrow I = 10 \angle -30^\circ \text{ A}$

(a)  $p(t) = |V||I| [\cos \phi + \cos(2\omega t + \angle V + \angle I)]$   
 $= 600 + 1200 \cos 2\omega t \text{ W}$

$S = VI^* = 1200 \angle 60^\circ = P + jQ \Rightarrow P = 600 \text{ W}, Q = 1039 \text{ VAR}$

(b)  $Z = V/I = 12 \angle 60^\circ = 6 + j10.39 = R + jX \Rightarrow R = 6, X = 10.39$

2.2 (a) Using (2.3) we find  $P_{\max} = 1707 = |V||I|(\cos \phi + 1)$   
 and  $P_{\min} = -293 = |V||I|(\cos \phi - 1)$ . Then, since  $|V| = 100$ , we  
 get  $|I| = 10$  and  $\cos \phi = \pm 45^\circ$ . Pick  $\phi = 45^\circ \Rightarrow Z = 10 \angle 45^\circ =$   
 $7.07 + j7.07 = R + jX \Rightarrow R = 7.07, X = 7.07$

(b)  $S = VI^* = Z|I|^2 = (7.07 + j7.07) 10^2 \Rightarrow P = 707, Q = 707$

(c) For simplicity assume  $i(t) = \sqrt{2}|I| \cos \omega t$ . Then  
 $p_L(t) = v_L(t) i(t) = L \frac{di}{dt} i = -2\omega L |I|^2 \cos \omega t \sin \omega t = -\omega L |I|^2 \sin 2\omega t$   
 $P_{L\max} = \omega L |I|^2 = 707 = Q$ . Thus  $P_{\max} = Q$ . The same!

2.3 0.7 PF lagging  $\Rightarrow \phi = 45.57^\circ, Q = 5.10 \text{ MVAR}$


0.9 PF lagging  $\Rightarrow \phi = 25.84^\circ, Q = 2.42 \text{ MVAR}$ . Capacitor must  
 supply  $5.10 - 2.42 = 2.68 \text{ MVAR}$ .

2.4 0.707 PF lagging  $\Rightarrow S_{3\phi} = 200 + j200 \text{ kVA}$ . Cap supplies  
 $50 \text{ kVAR}$ . Resultant  $S_{3\phi} = 200 + j150 \text{ kVA} \Rightarrow PF = 0.80$ .

$|S| = \frac{|S_{3\phi}|}{3} = \frac{250 \times 10^3}{3} = |V||I| = \frac{440}{\sqrt{2}} |I| \Rightarrow |I| = 328 \text{ A}$

2.5 0.9 PF lagging  $\Rightarrow \phi = 25.84^\circ$

(a)  $S = 10 + j4.84 \text{ kVA}$

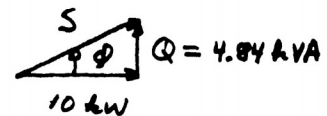

(b)  $10 \times 10^3 = 416 \times |I| \times 0.9 \Rightarrow |I| = 26.71 \text{ A}$

(c) Using (2.3), (or first principles) we get

$p(t) = 10 \times 10^3 + 11.11 \times 10^3 \cos(2\omega t + 25.84^\circ)$

Note: the average value of  $p(t)$  is  $10 \text{ kW}$

2.6 Because system is balanced  $V_{ab} = 208 \angle 120^\circ$ ,  $V_{bc} = 208 \angle 0^\circ$ .  
 Using (2.17) or Fig 2.11,  $V_{an} = 120 \angle 90^\circ \Rightarrow V_{bn} = 120 \angle -30^\circ$ ,  
 $V_{cn} = 120 \angle -150^\circ$ . Using per phase analysis,  $I_a = 12 \angle 105^\circ \Rightarrow$   
 $I_b = 12 \angle -15^\circ$ ,  $I_c = 12 \angle -135^\circ$ .

2.7  $S = VI^* = V(YV)^* = Y^* M^2 = Y_C^* + Y_L^* + Y_R^*$   
 $= -j5 + j10 + 0.1 = 0.1 + j5$

2.8 (a) Using loop or nodal analysis we find, after much work,  
 $I_a = 0.9123 \angle -90.351^\circ$ ,  $I_b = 0.9123 \angle -209.65^\circ$ ,  $I_c = 0.9929 \angle 30^\circ$ .

(b) Using per phase analysis  $I_a = 1 \angle 0^\circ / j1.1 = 0.9091 \angle -90^\circ$ ,  
 then,  $I_b = 0.9091 \angle -210^\circ$ ,  $I_c = 0.9091 \angle 30^\circ$ .

2.9 Proceeding by analogy with  $3\phi$ , we note


$$E_{ab} = E_{an} - E_{bn} = E_{an}(1 - e^{-j\pi/2}) = \sqrt{2} E_{an} e^{j\pi/4}$$

Thus  $E_{an} = \frac{1}{\sqrt{2}} E_{ab} e^{-j\pi/4}$ , and  $E_{an}, E_{bn}, E_{cn}, E_{dn}$  form  
 a pos. seq. set of  $4\phi$  voltages. Doing per phase (phase a)  
 analysis we have

$$\frac{1}{\sqrt{2}} \angle 45^\circ \text{ (circuit diagram)} - j0.5 \Rightarrow I_a = \frac{\frac{1}{\sqrt{2}} \angle -45^\circ}{j0.5} = \sqrt{2} \angle -135^\circ$$

Then  $I_b = \sqrt{2} \angle -225^\circ$ ,  $I_c = \sqrt{2} \angle -315^\circ$ ,  $I_d = \sqrt{2} \angle -405^\circ$

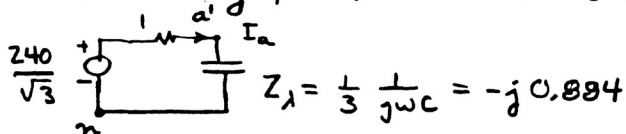2.10 Using per phase circuit we find  $I_a = 103.8 \angle 41.5^\circ$ .



Then  $|I_b| = 103.8 \text{ A}$


$$V_{a'n} = Z_1 I_a = 91.76 \angle -48.5^\circ \Rightarrow |V_{a'b'}| = \sqrt{3} \cdot 91.76 = 158.9 \text{ V}$$

$$S_{\text{load}} = V_{a'n} I_a^* = 9524 \angle -90^\circ$$

$$S_{\text{load}}^{3\phi} = 3 S_{\text{load}} = 28574 \angle -90^\circ \text{ W}$$

2.11 Assume pos. seq. operation.  $V_{a''b''} = V_{a''n} - V_{b''n} = \sqrt{3} V_{a''n} e^{j\pi/6} \Rightarrow V_{a''n} = \frac{1}{\sqrt{3}} V_{a''b''} e^{-j\pi/6} = \frac{1}{\sqrt{3}} \angle -30^\circ$

Per Phase Ckt

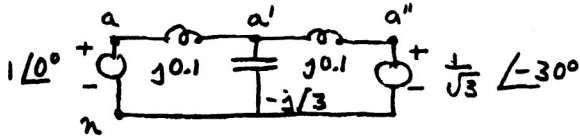


Using superposition & voltage divider law we get

$V_{a'n} = 0.899 \angle -10.89^\circ \Rightarrow V_{b'n} = 0.899 \angle -130.89^\circ$  and

$V_{c'n} = 0.899 \angle -250.89^\circ$ . Then  $V_{a'b'} = 1.557 \angle 19.11^\circ$

2.12 Assume pos. seq..

Per Phase Ckt

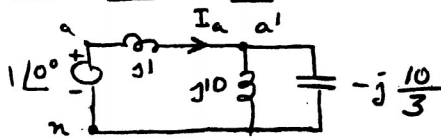

Combining parallel elements we have  $Z_{||} = -j5$ .  $I_a = 0.25 \angle 90^\circ$

$V_{a'n} = -j5 \cdot j0.25 = 1.25 \angle 0^\circ$

$V_{b'b'} = 2.165 \angle 30^\circ \Rightarrow I_{cap} = 0.2165 \angle 120^\circ$

$I_{load} = 3 V_{a'n} I_a^* = 0.3125 \angle -90^\circ$

2.13

(a)  $V_{bc} = 208 \angle -120^\circ$ ,  $V_{ca} = 208 \angle 120^\circ$

$V_{an} = \frac{208}{\sqrt{3}} \angle -30^\circ \Rightarrow I_a = 1.20 \angle -90^\circ$


Then  $I_b = 1.20 \angle -210^\circ$ ,  $I_c = 1.20 \angle -330^\circ$

(b)  $V_{bc} = 208 \angle 120^\circ$ ,  $V_{ca} = 208 \angle -120^\circ$

$V_{an} = \frac{208}{\sqrt{3}} \angle 30^\circ \Rightarrow I_a = 1.20 \angle -30^\circ$

$I_b = 1.20 \angle 90^\circ$ ,  $I_c = 1.20 \angle -150^\circ$

2.14 Per Phase Ckt. Problem reduces to picking  $Z$  so that  $|V_{a'n}| > |V_{an}|$ . It helps to draw some phasor diagrams.

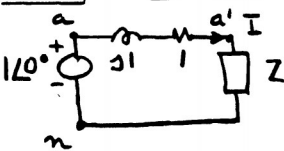

I. $Z = j\omega L$	II. $Z = R$	III. $Z = -j/\omega C$
<p>clearly <math> V_{a'n}  &lt;  V_{an} </math></p>	<p>clearly <math> V_{a'n}  &lt;  V_{an} </math></p>	<p>For example <math>Z = -j2</math>  <math>I = \frac{1}{\sqrt{2}} \angle 45^\circ</math>  <math>V_{a'n} = \sqrt{2} \angle -45^\circ</math>  <math> V_{a'n}  &gt;  V_{an} </math>                      this is o.k.</p>