
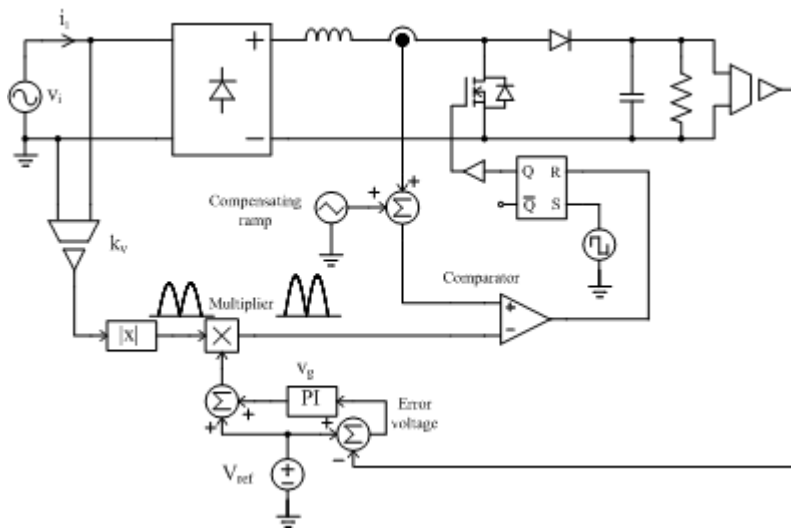


# Chapter 13

## Applications of switching converters

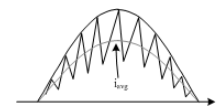



# Power factor correction

- Review of basic concepts

$$S = V_{rms} I_{rms}$$


$$P = \text{Re}(S) = V_{rms} I_{rms} \cos(\varphi)$$

$$PF = \frac{P}{S}$$

$$i(t) = i_1(t) + \sum_{h \neq 1} i_h(t)$$

$$I_{rms} = \sqrt{\sum_{h=1} I_h^2}$$


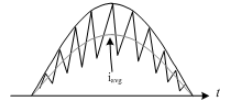
$$PF = \frac{P}{S} = \frac{V I_1 \cos(\varphi)}{V I} = \frac{I_1}{I} \cos(\varphi)$$




# Principle of power factor correction

The main goal of a power factor correction (PFC) circuits is to force the load to draw a quasi-sinusoidal current from the AC power line to be in phase with the line voltage; thus, behaving as a resistive load or a controlled current source to the AC mains.

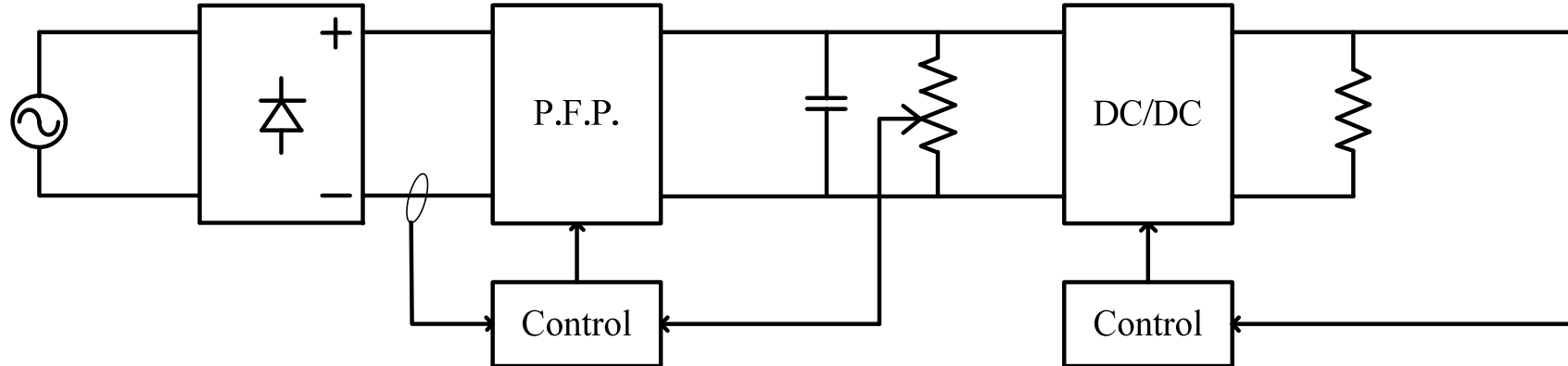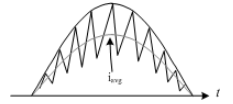
# Block diagram of a typical AC-DC converter with a power factor pre-regulator



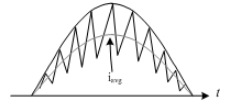
# Self-power factor correction properties of switching converters



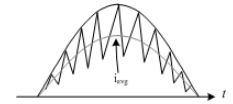- Switching converters exhibit self-power factor correction characteristics when operating in their discontinuous mode




# Buck converter

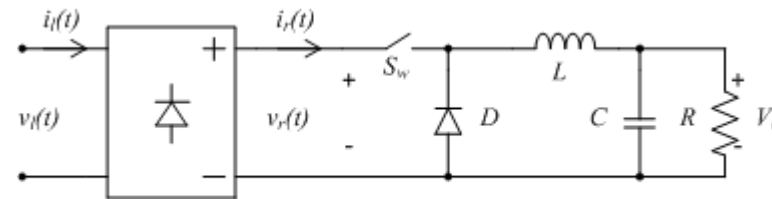


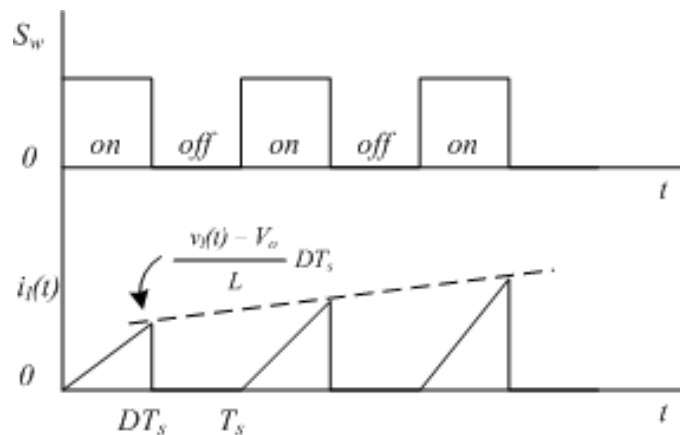a) Buck converter.


$$i_{l,avg}(t) = \frac{1}{T_s} \left[ \frac{1}{2} D T_s \frac{v_l(t) V_o}{L} D T_s \right] = \frac{D^2 T_s}{2L} v_l(t) - \frac{D^2 T_s}{2L} V_o$$




b) Input current.

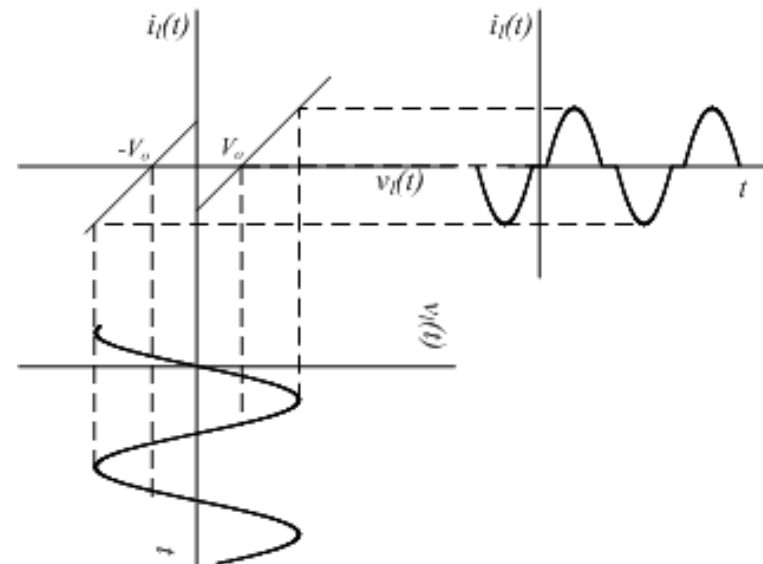

c) Input V-I characteristic.

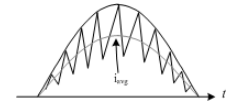


# Boost converter

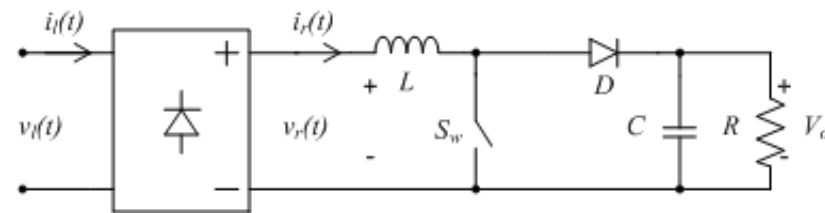


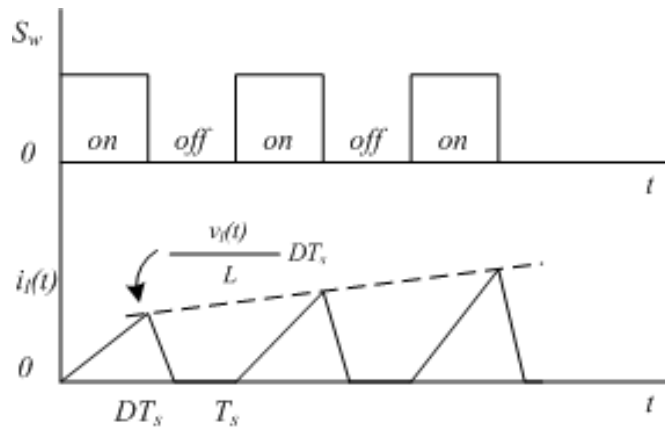a) Boost converter.


$$i_{l,avg}(t) = \frac{1}{T_s} \left[ \frac{1}{2} (D + D_1) T_s \frac{v_l(t)}{L} D T_s \right] = \frac{D^2 T_s}{2L} \frac{v_l(t) V_o}{V_o - v_l(t)}$$




b) Input current.

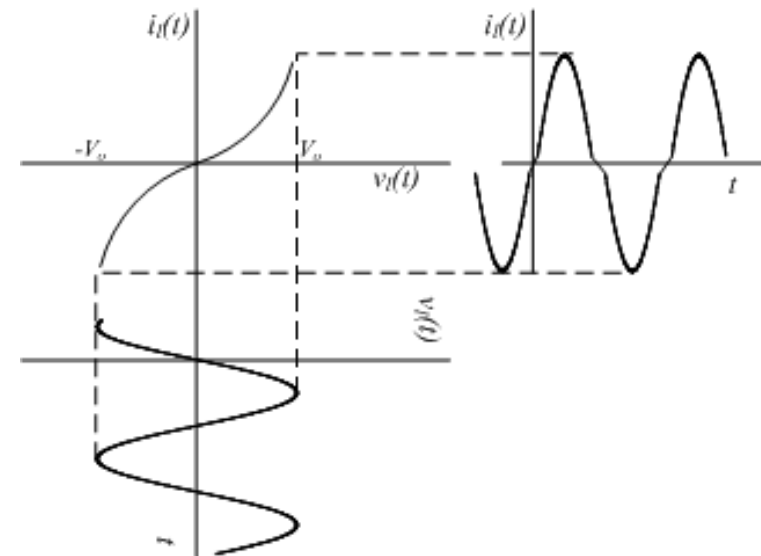

c) Input V-I characteristic.

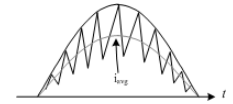


# Buck-boost converter

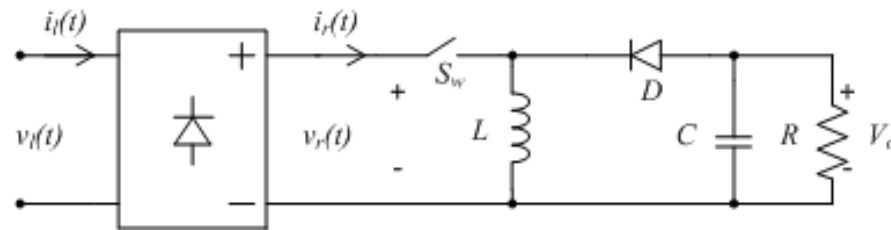


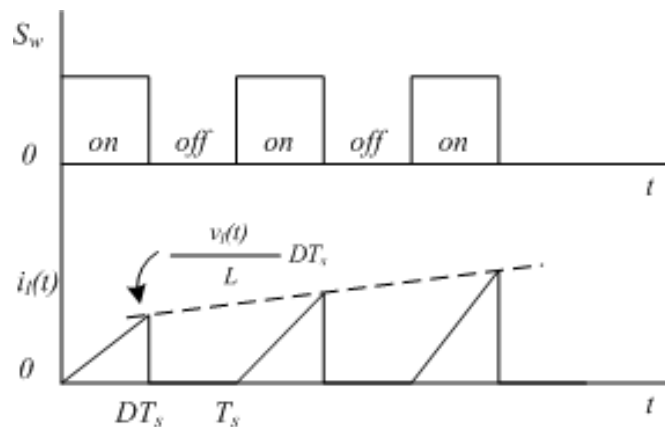a) Buck-boost converter.

$$i_{l,avg}(t) = \frac{D^2 T_s}{2L} v_l(t)$$




b) Input current.

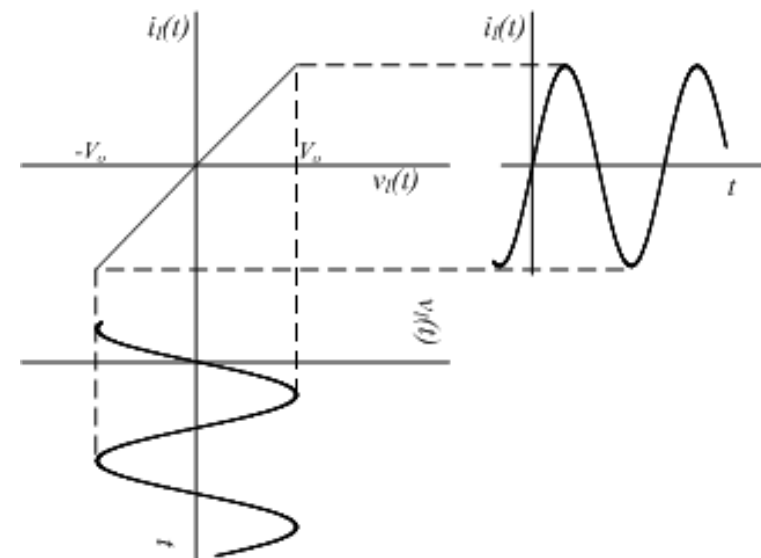


c) Input V-I characteristic.



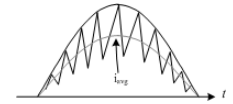


# Flyback converter

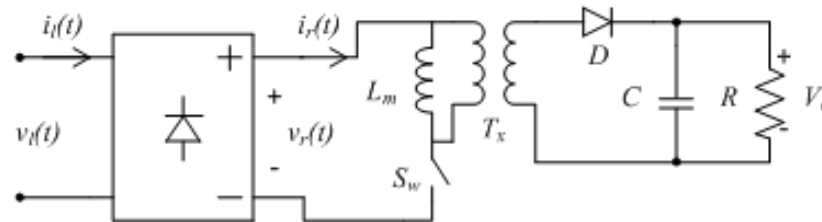


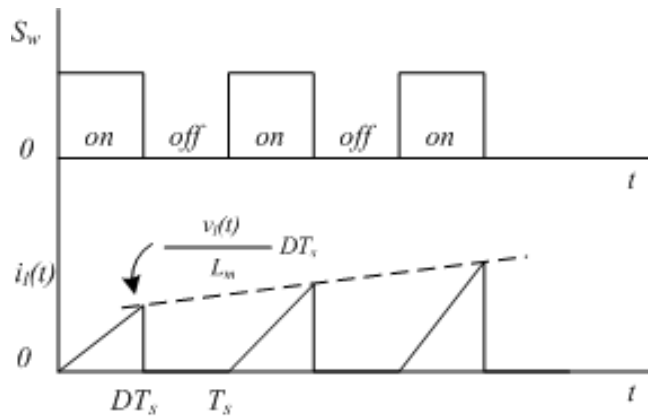a) Flyback converter.

$$i_{l,avg}(t) = \frac{D^2 T_s}{2 L_m} v_l(t)$$




b) Input current.

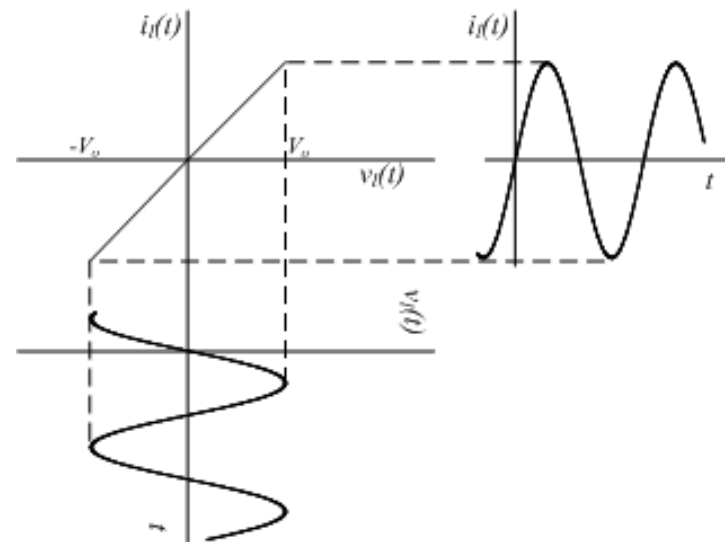


c) Input V-I characteristic.
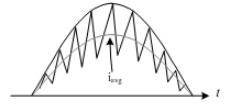
# Control techniques for power factor correctors





- Continuous conduction mode (CCM)
- Discontinuous conduction mode (DCM)
- Boundary conduction mode (BCM)
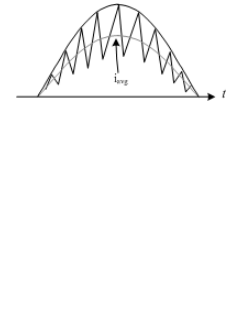
# Control techniques for power factor correctors




- Peak current mode control (PCM)
- Average current mode control
- Hysteresis control

# Peak current mode control (PCM)

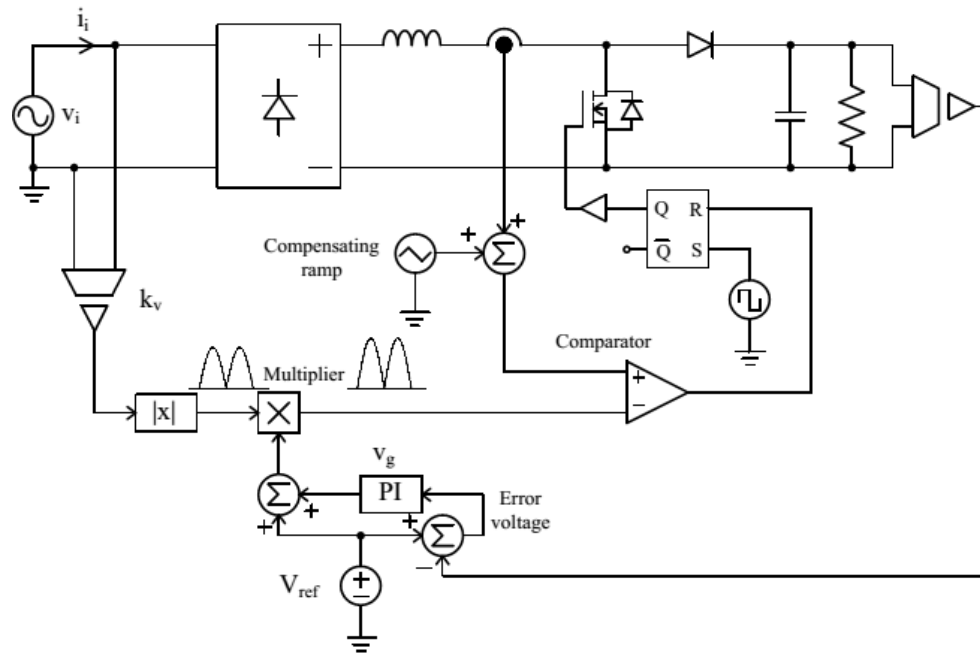
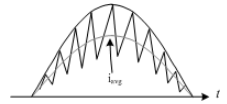


a) Schematic diagram.

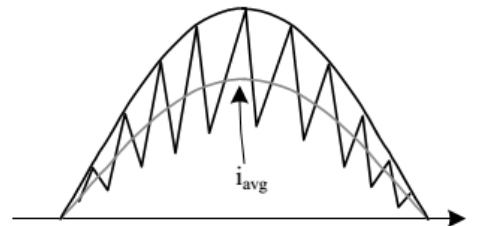


b) Current waveform.

# Average current mode control

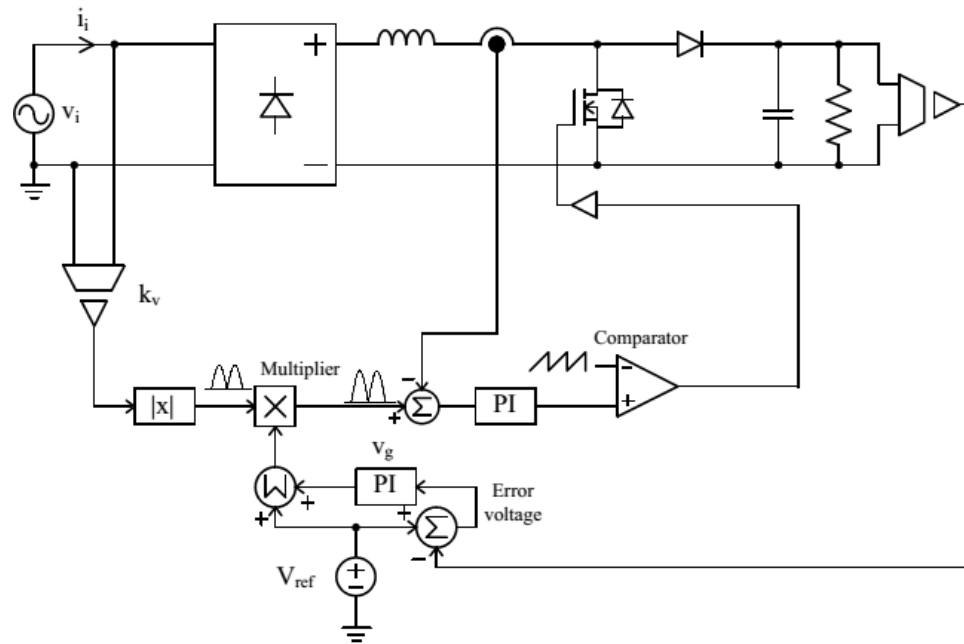
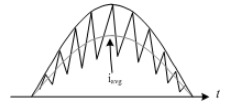


a) Schematic diagram.

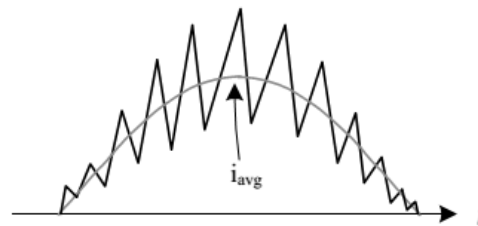


b) Current waveform.

# Hysteresis control

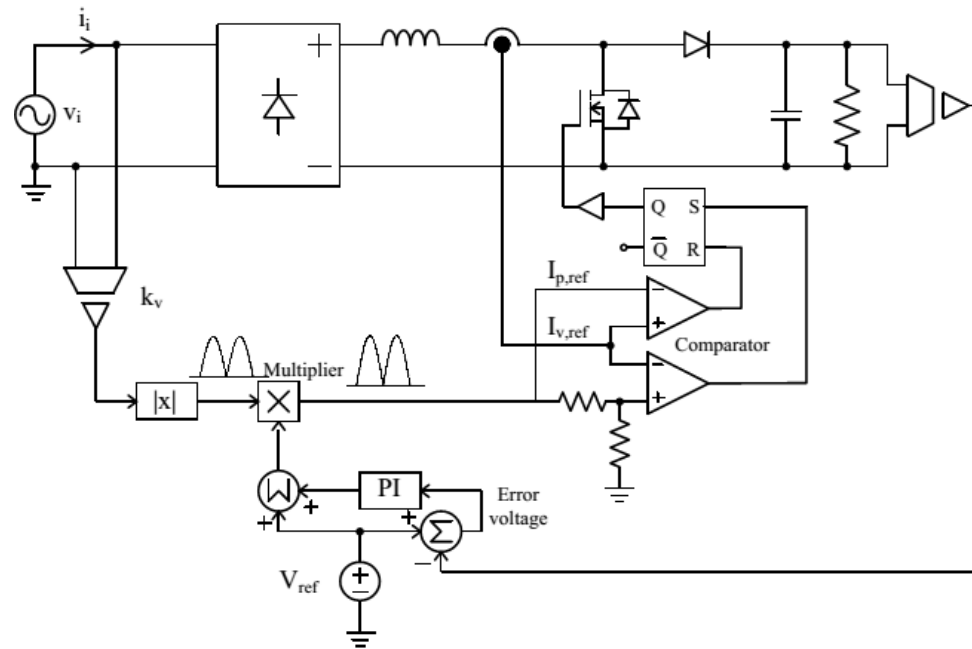
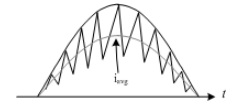


a) Schematic diagram.

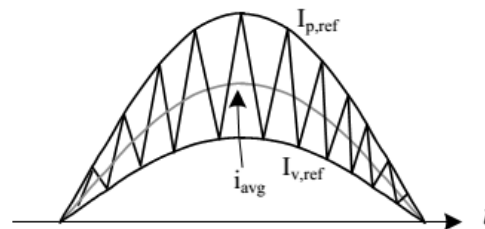


b) Current waveform.

# Borderline or boundary control

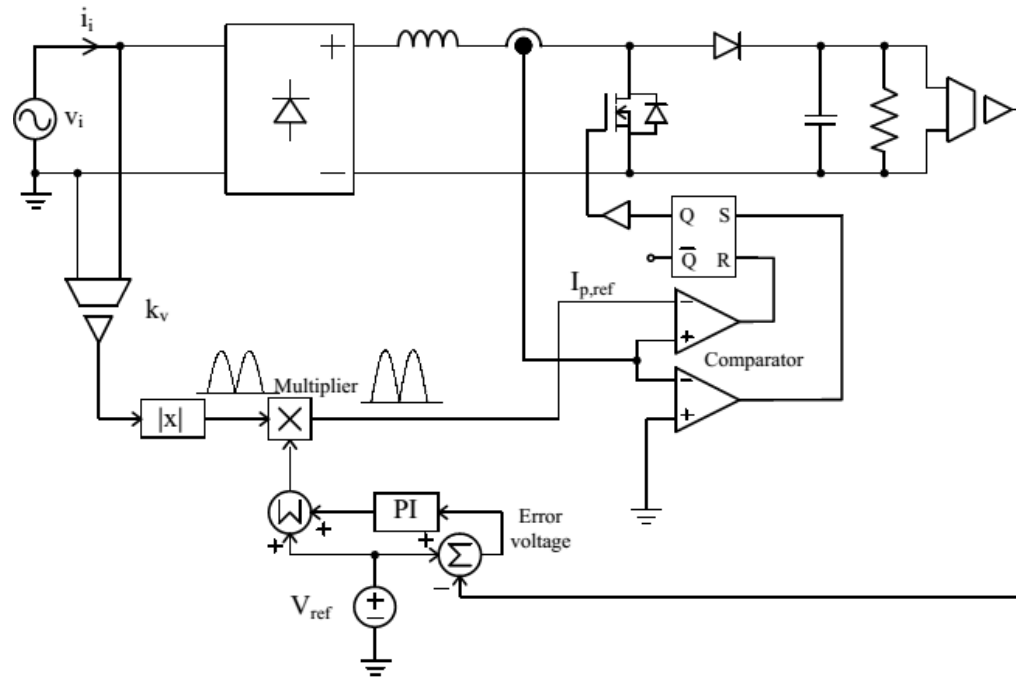
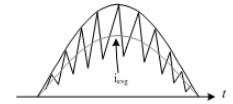


a) Schematic diagram.

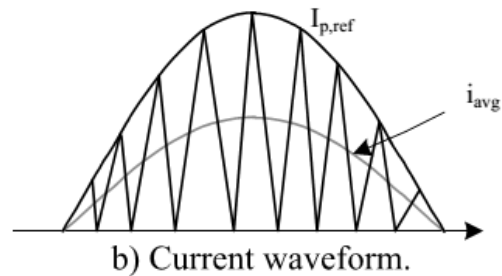


b) Current waveform.

# Discontinuous current PWM control

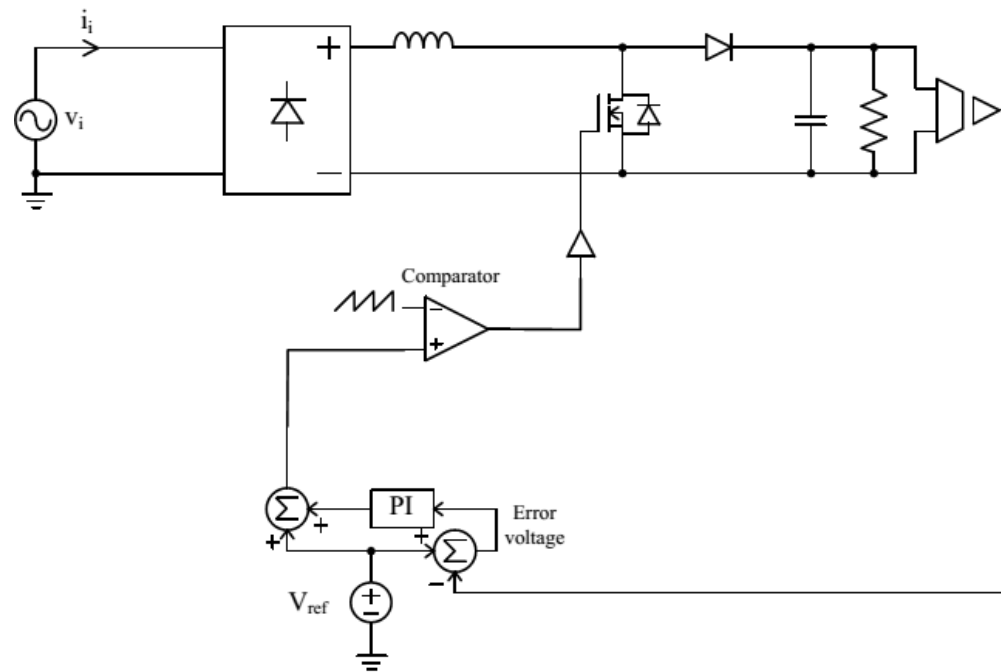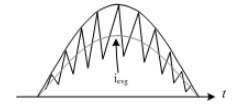




a) Schematic diagram.

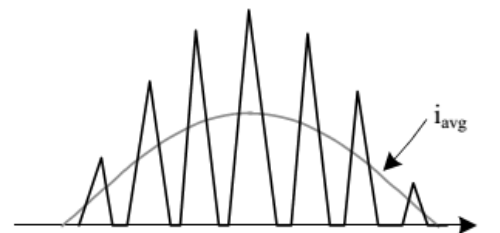

b) Current waveform.






# Power factor correction circuits

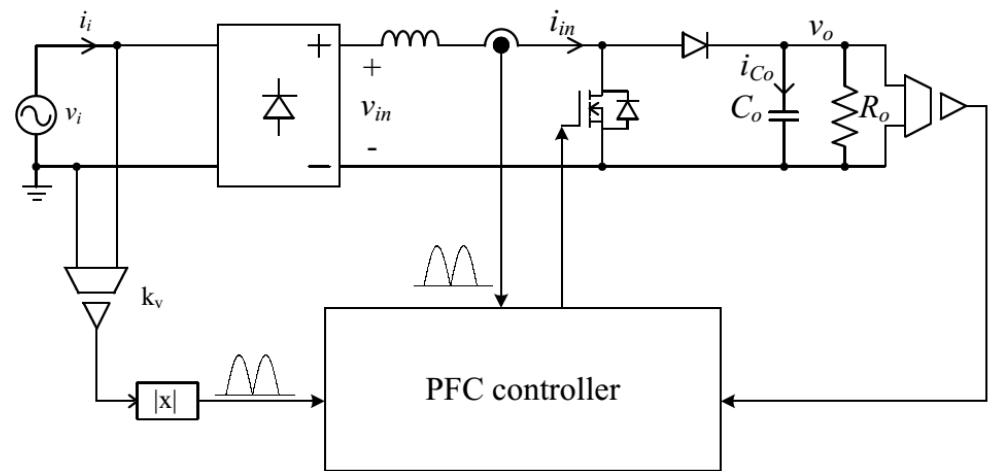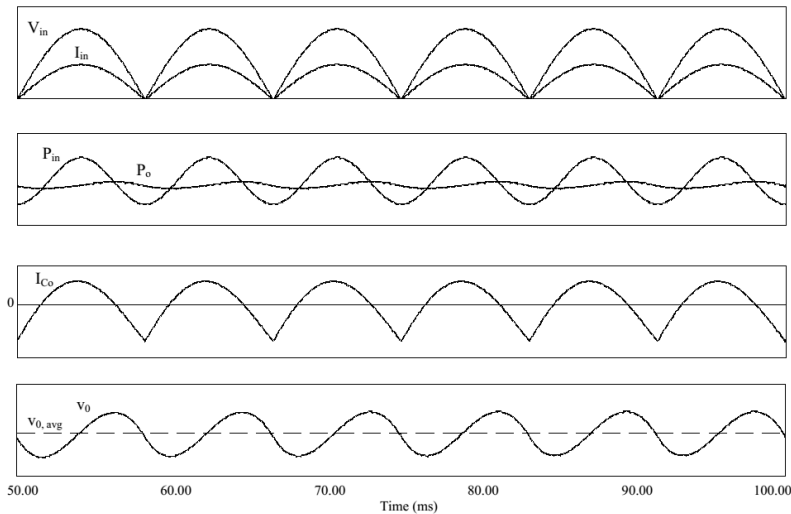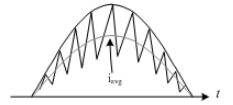

Basic boost-based PFC circuit

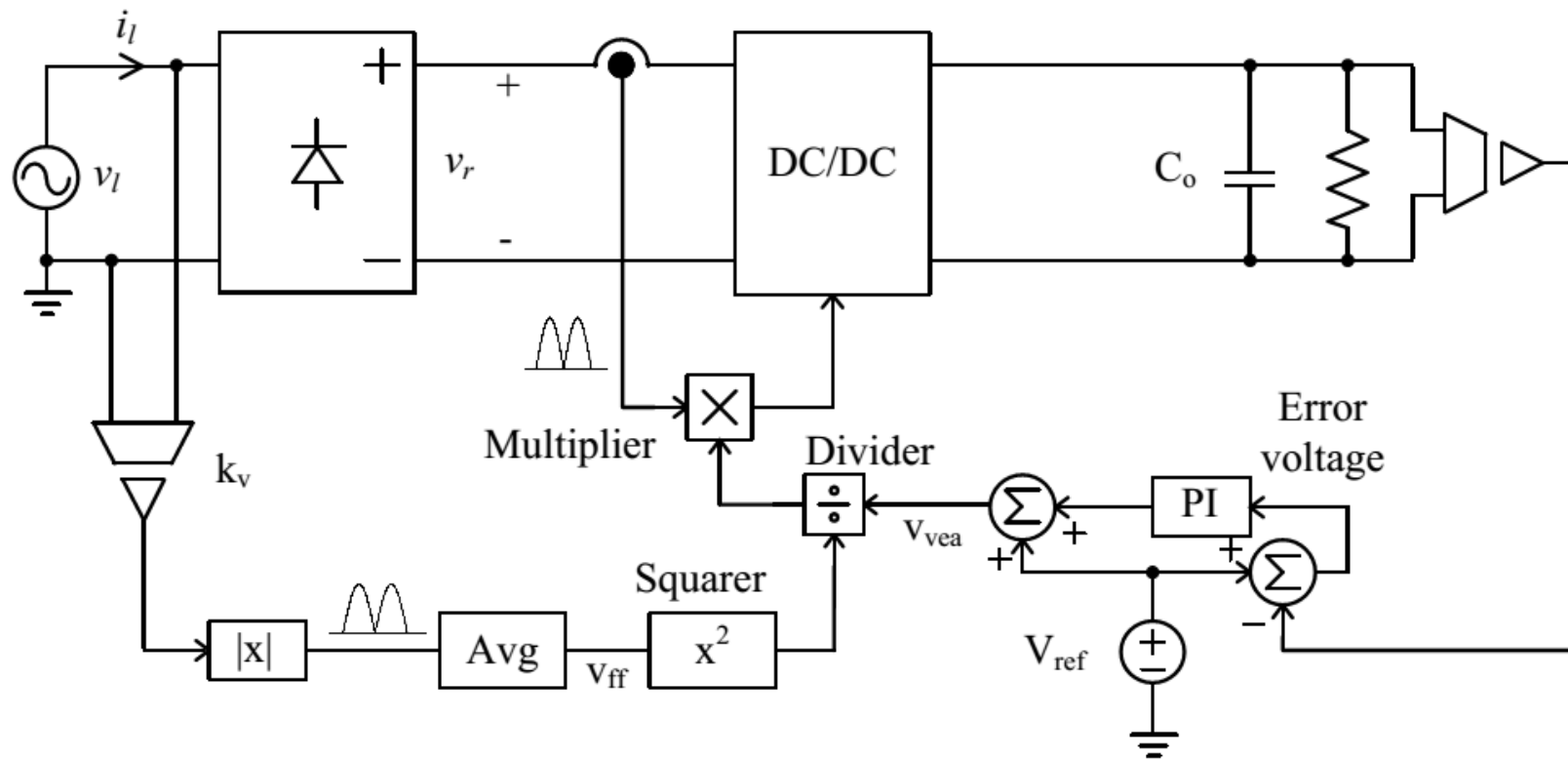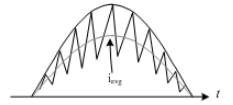
# A practical AC-DC converter with power factor correction



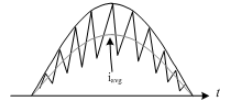
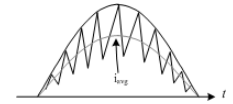
# Low noise DC-DC converters



- Linear power supplies produce low EMI but have low power efficiency
- Switched mode power supplies have higher power efficiency but produce EMI
- Low noise switching power supplies use several techniques to reduce the conducted and radiated EMI while achieving acceptable power efficiency




# Techniques to reduce EMI

- Capacitive coupling
- Inductive coupling
- Input filtering
- Output Filtering
- Slew rate limiting
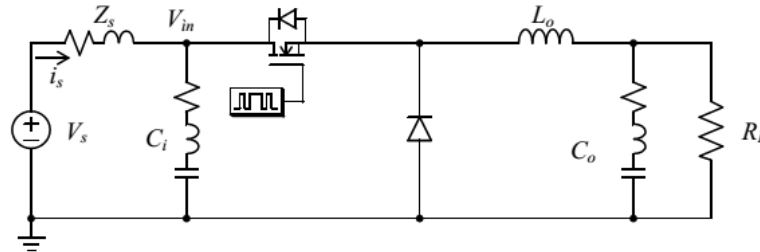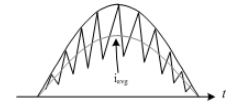
# Buck converter with practical input and output capacitors





a) Schematic diagram.

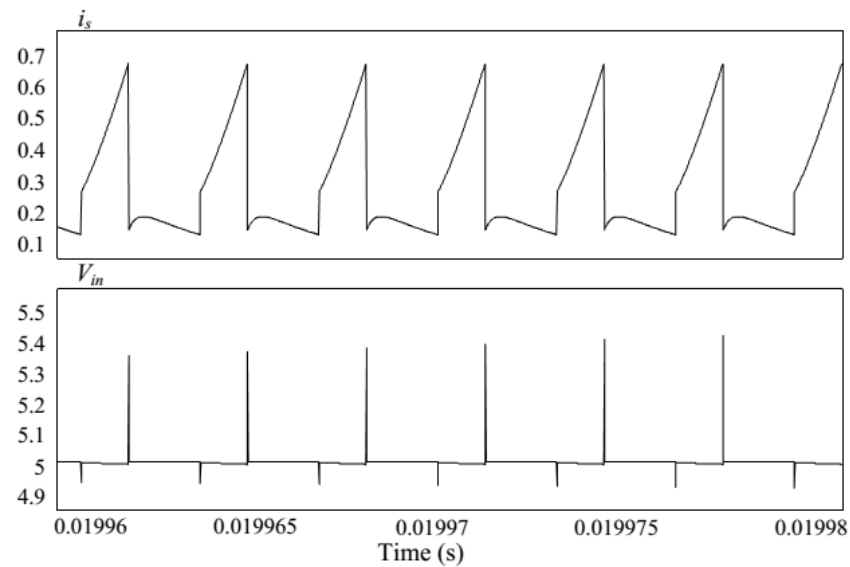


b) Input waveforms.
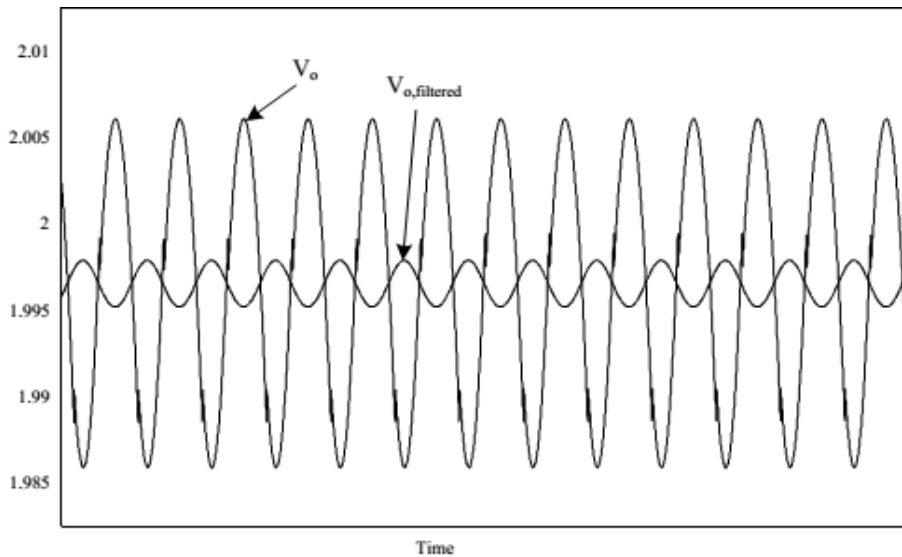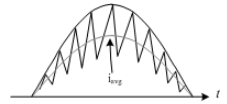
# Comparison of performance between one and two output filters





a) Waveforms.

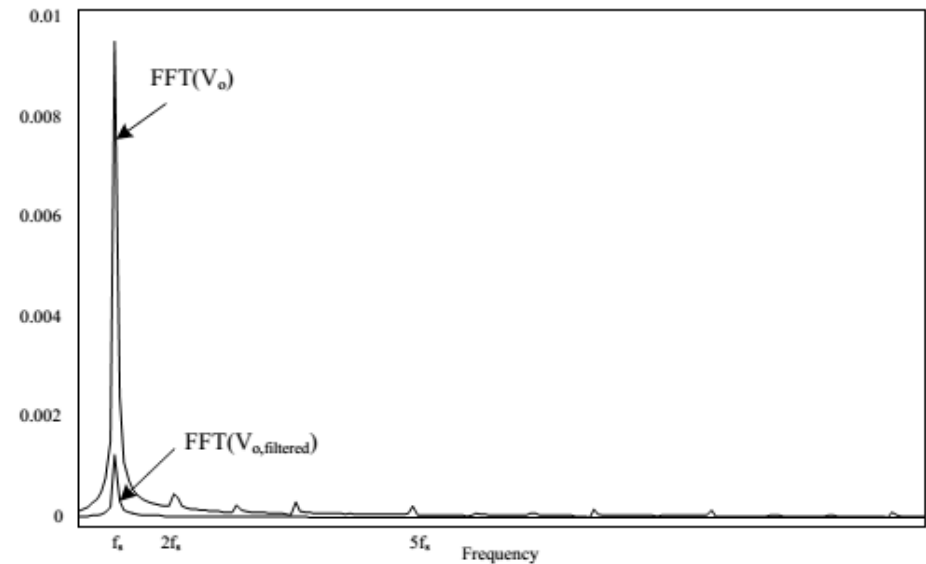


b) Frequency spectrum.
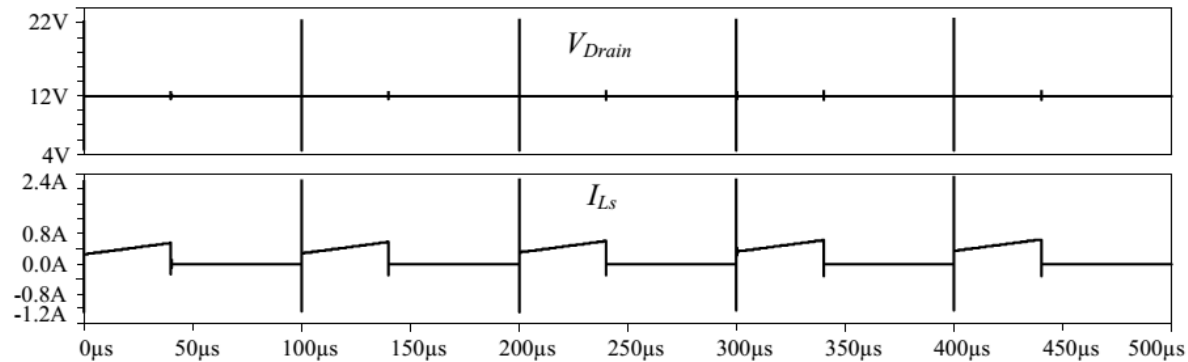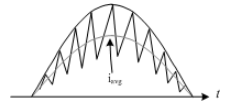
# Comparison of voltage waveforms with and without slew rate limitation




a) 10-ns rise time.

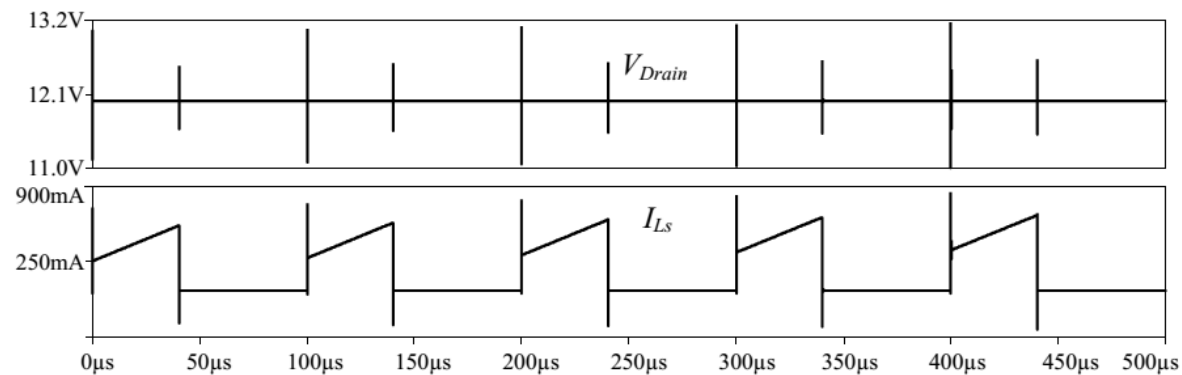


b) 100-ns rise time.


# Switching converters for solar cells

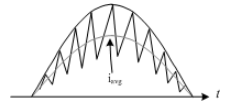


Typical configurations of PV systems

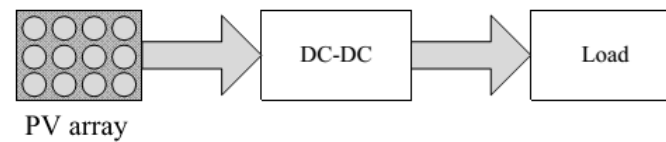

a) Isolated DC load.

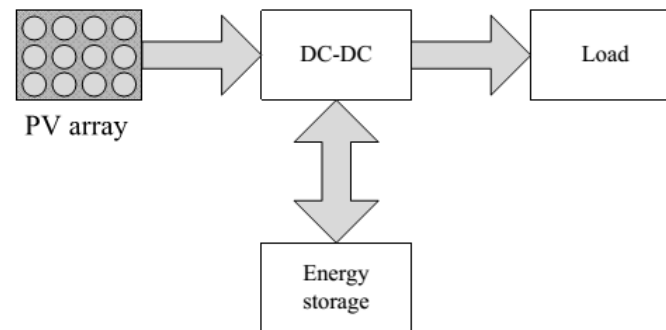


b) isolated DC load with energy storage.

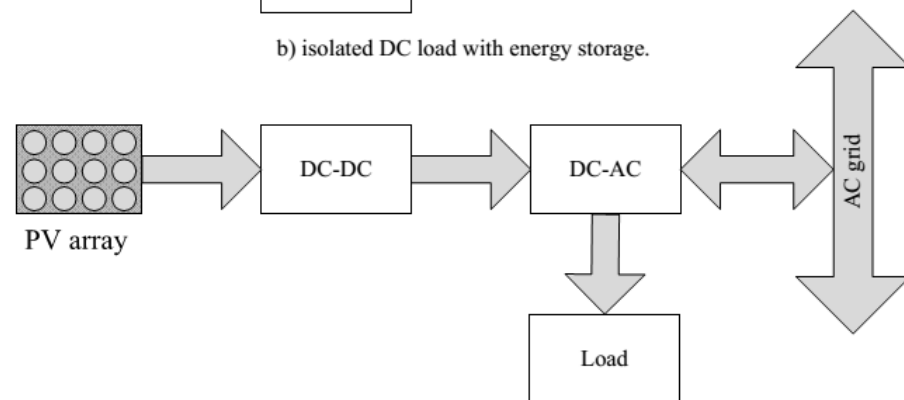


c) Grid connected AC load.




# Solar cell model

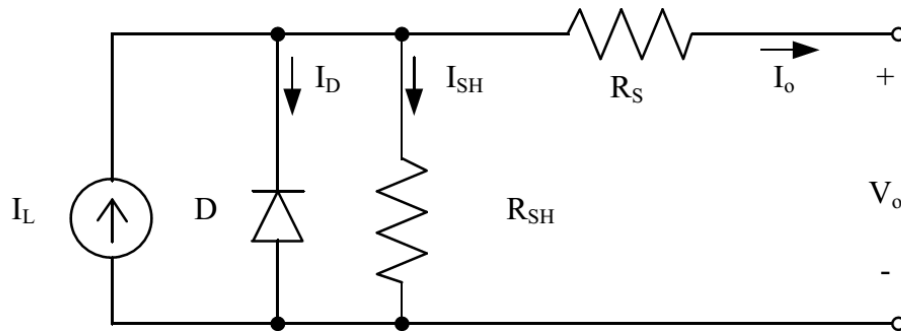



Equivalent circuit of a solar cell

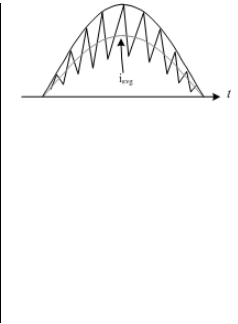

## I-V and power curves of a solar cell


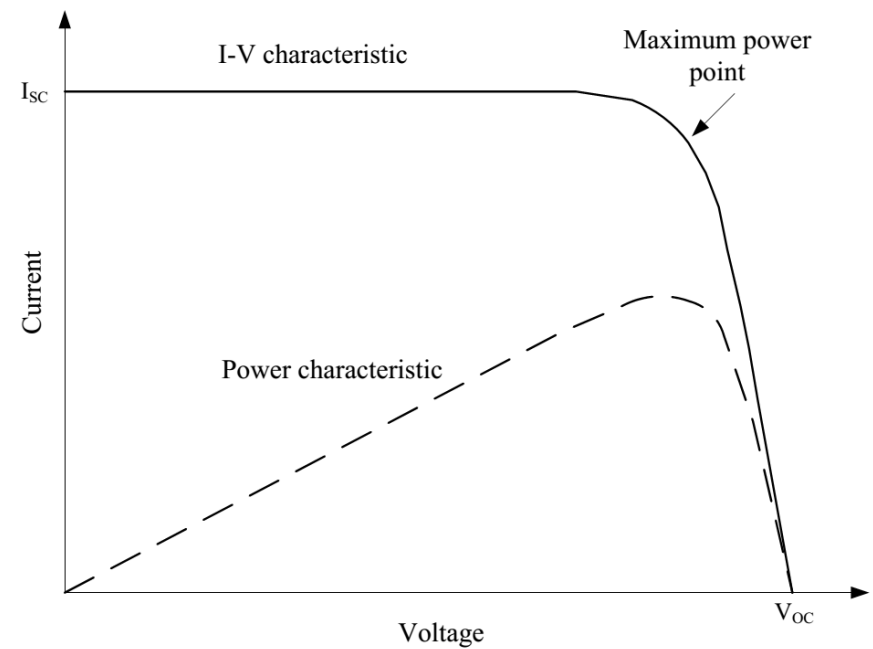


# Switching converters for fuel cells

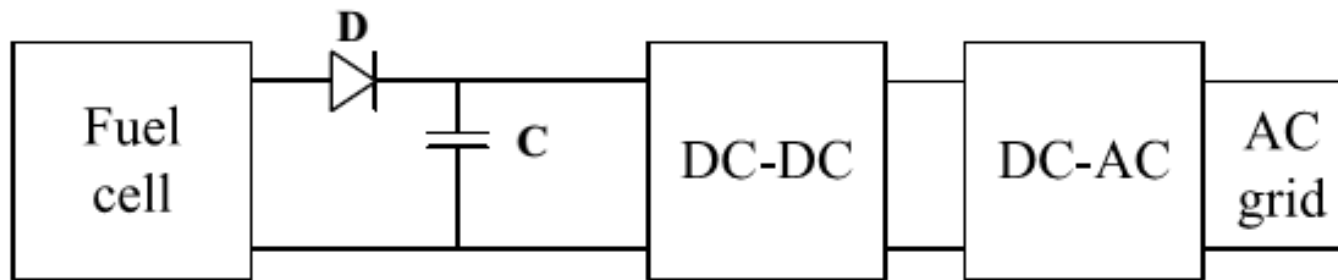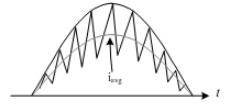


Block diagram representation of a fuel cell system

# Switching converters for fuel cells

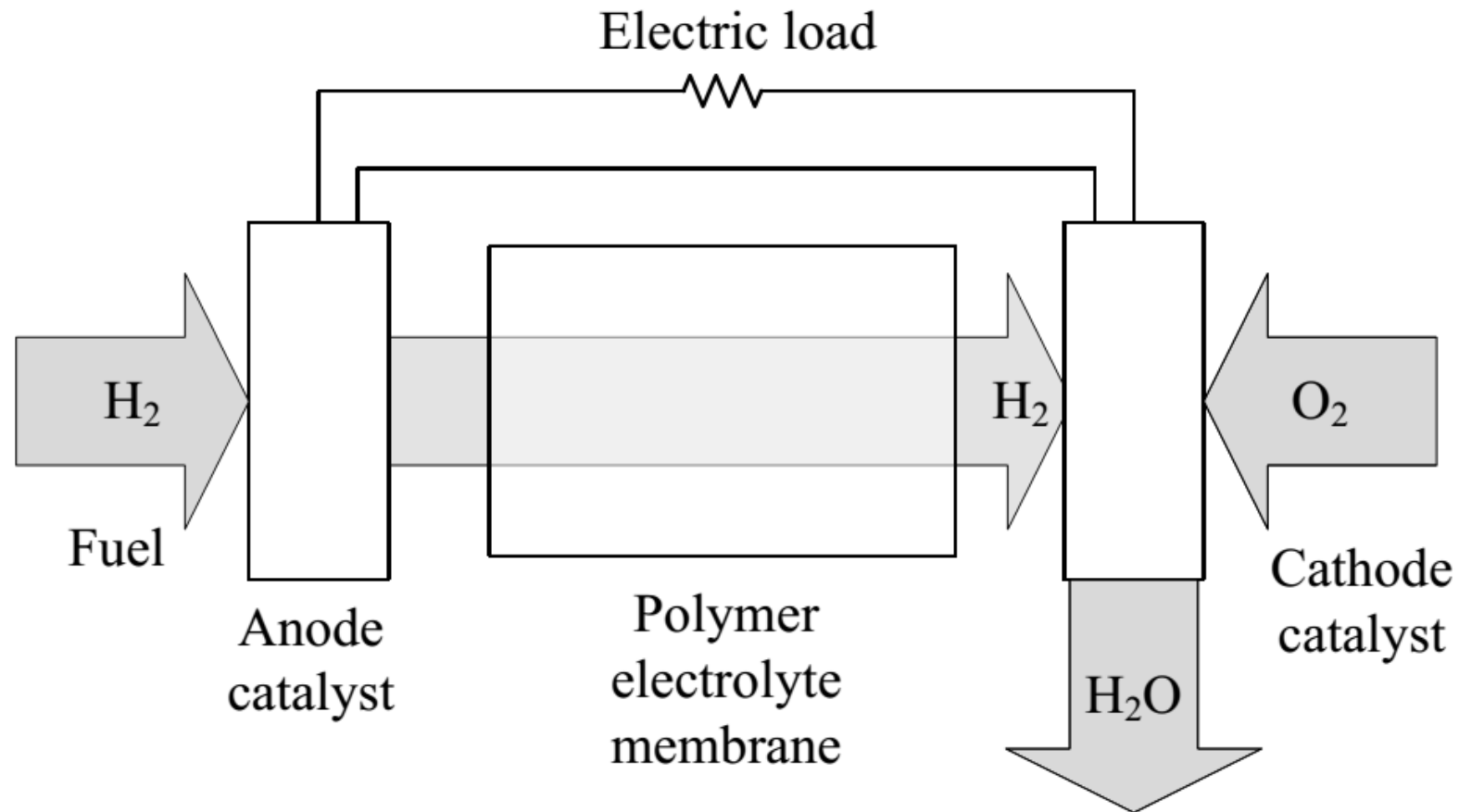
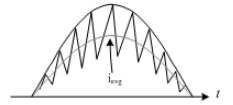


Block diagram of a fuel cell


# Switching converters for fuel cells

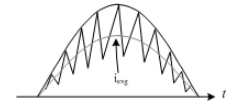

Equivalent circuit of a fuel cell

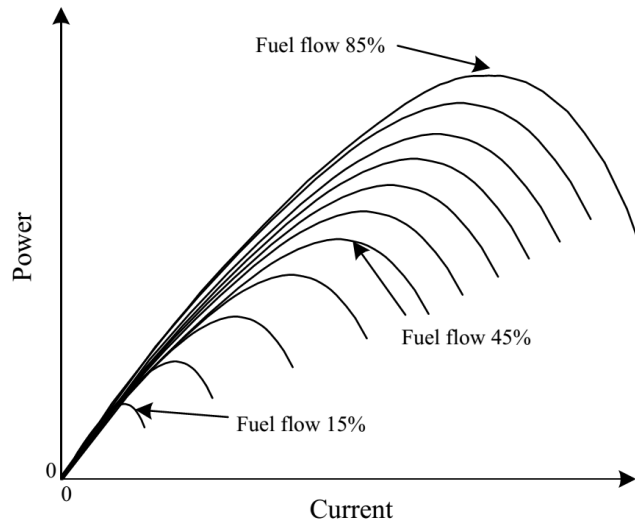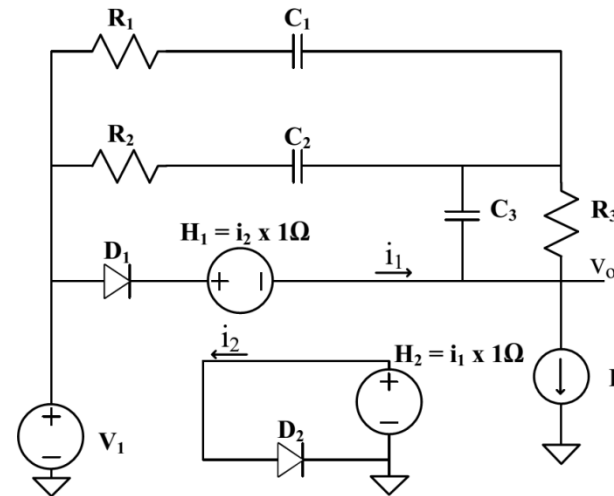


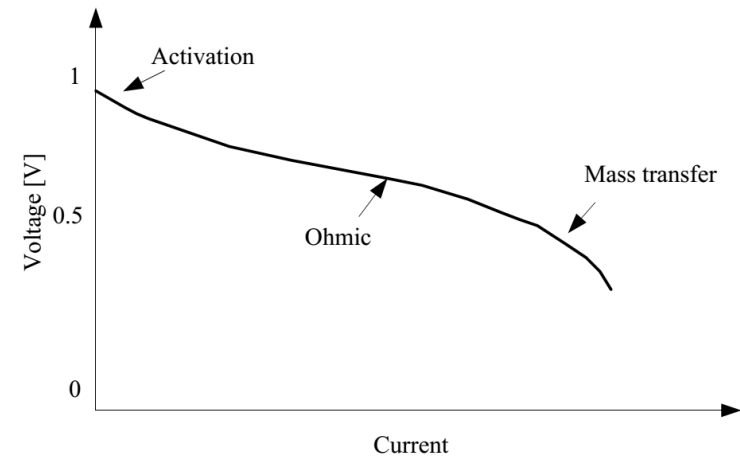Power-current characteristic of a fuel cell





Voltage-current characteristic of a fuel cell


# Switching converters for LED drivers

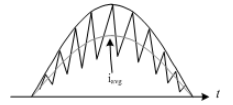


## Buck-based LED drivers

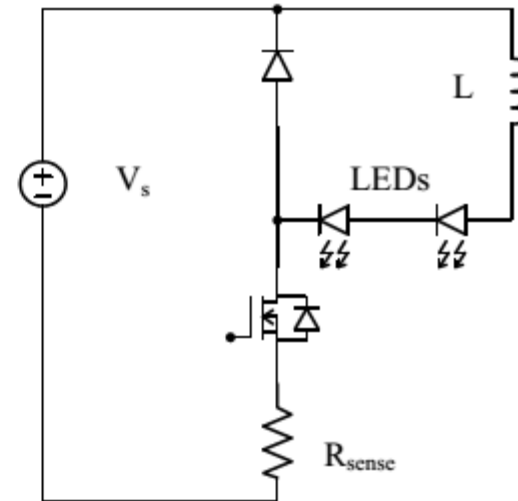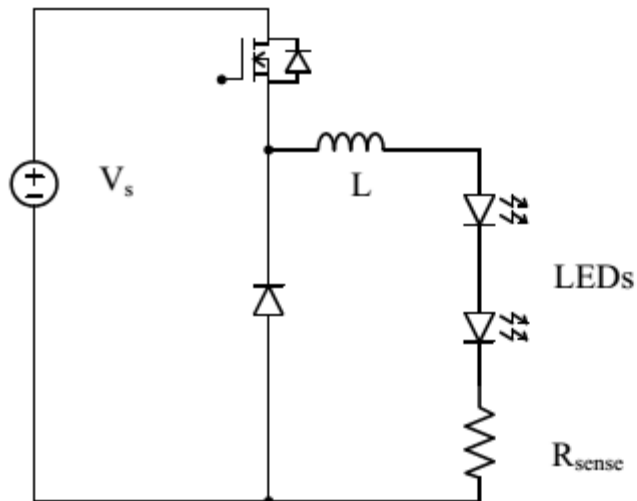


# Switching converters for LED drivers

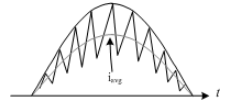

## Boost-based LED drivers

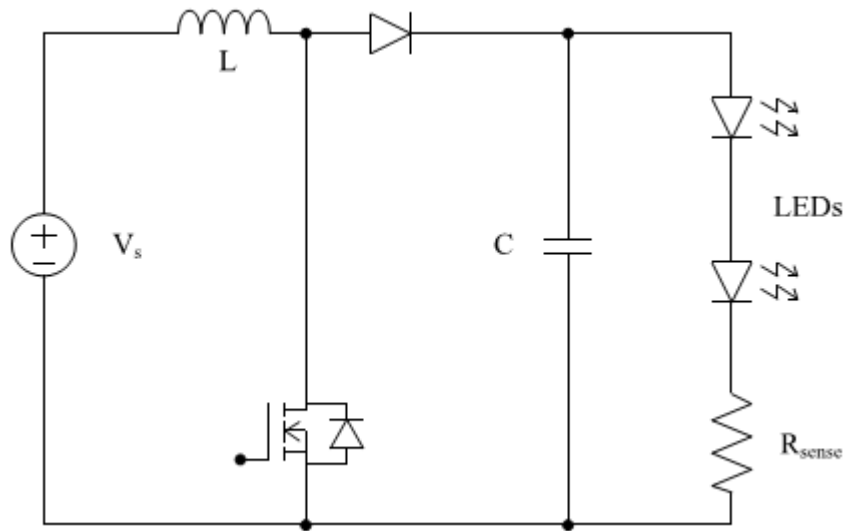

# Switching converters for LED drivers

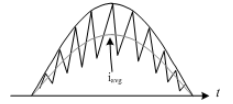

## Cuk-based LED drivers

