

Figure 2.1  
Ideal diode.

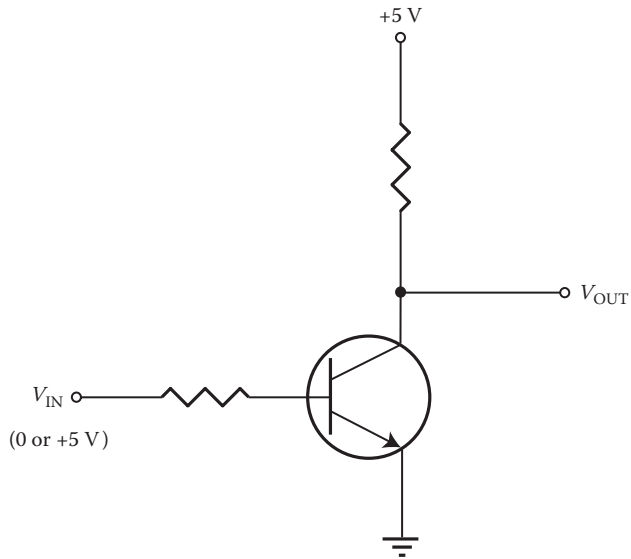


Figure 2.2  
An example of a transistor inverter.

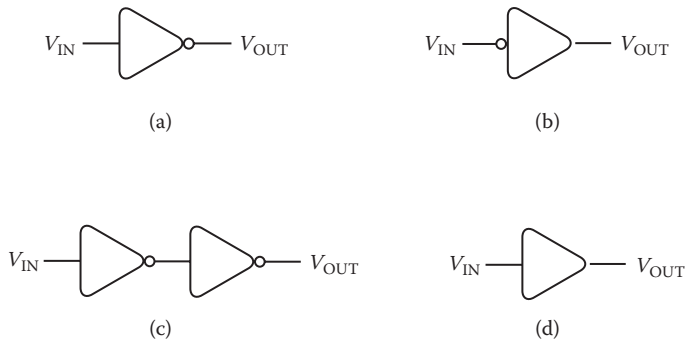


Figure 2.3

Logic symbols: (a) active-HIGH input inverter, (b) active-LOW input inverter, (c) double inverter, (d) buffer.

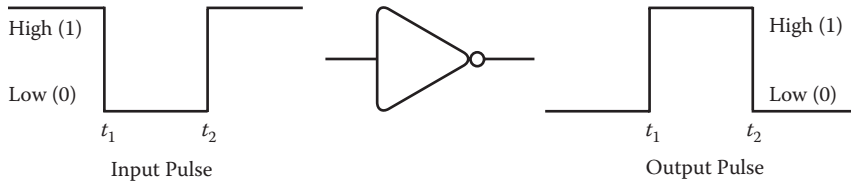


Figure 2.4  
Inverter operation with a pulse input.

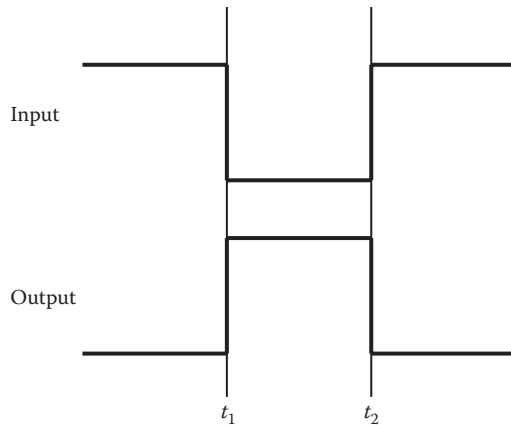


Figure 2.5  
Timing diagram for Figure 2.4.



Figure 2.6  
Timing diagram for Example 2.1.

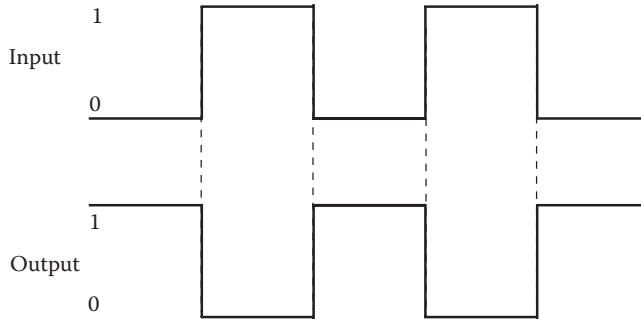


Figure 2.7  
Timing diagram solution for Example 2.1.



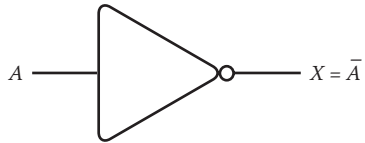


Figure 2.8  
Logic expressions for an inverter.

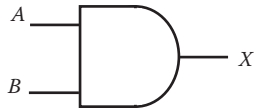


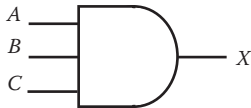

(a)



(b)

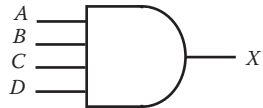

(c)

Figure 2.9  
AND gate symbols.



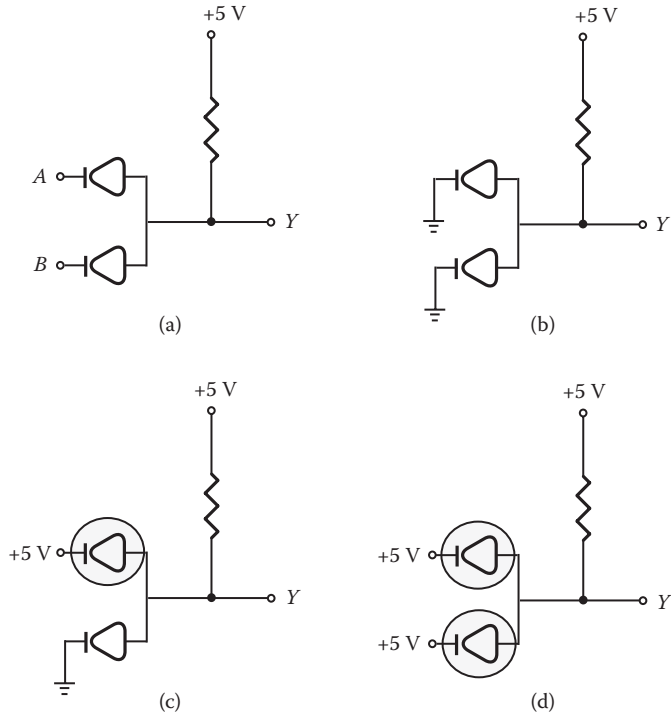



Figure 2.10  
A simple AND gate construction with various scenarios.

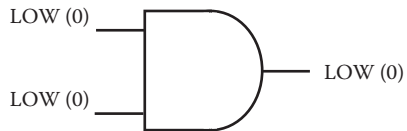


(a)

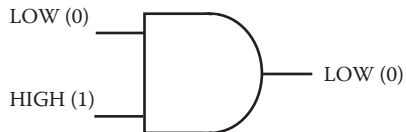

(b)

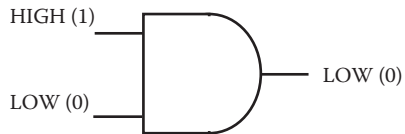

(c)

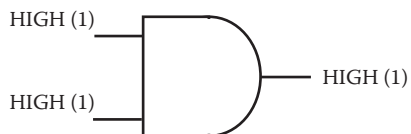

(d)

Figure 2.11  
Operation of a 2-input AND gate.

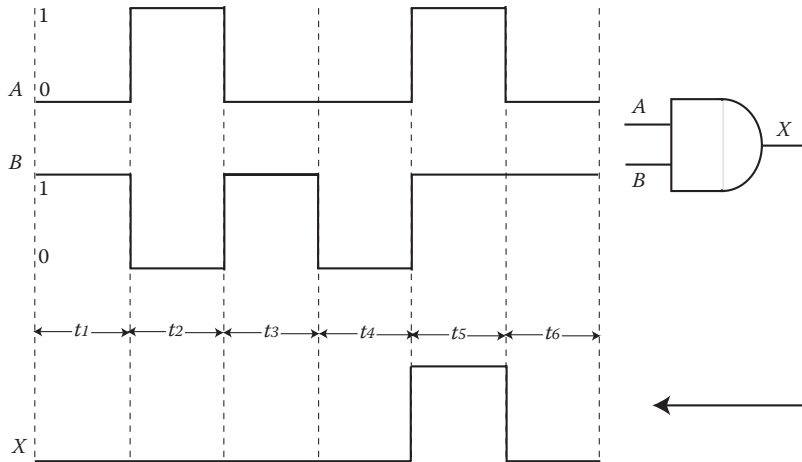


Figure 2.12  
Example of an AND Gate operation with a timing diagram showing input and output relationships.

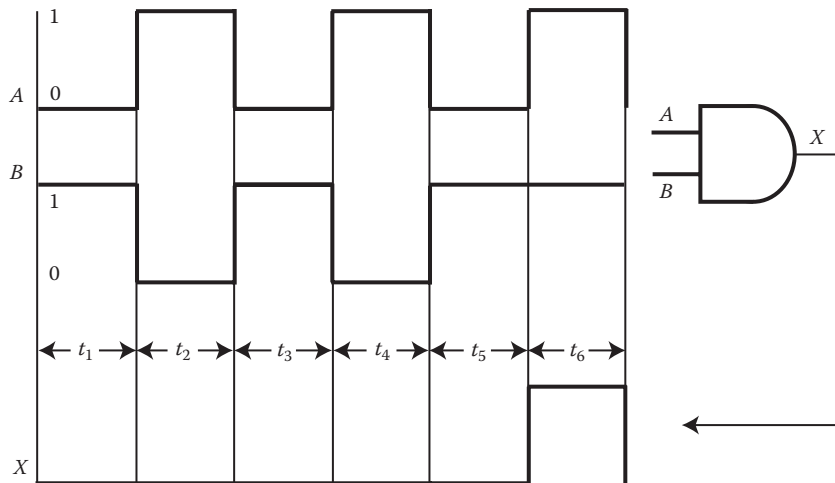


Figure 2.13  
Timing diagram for a 2-input AND gate.



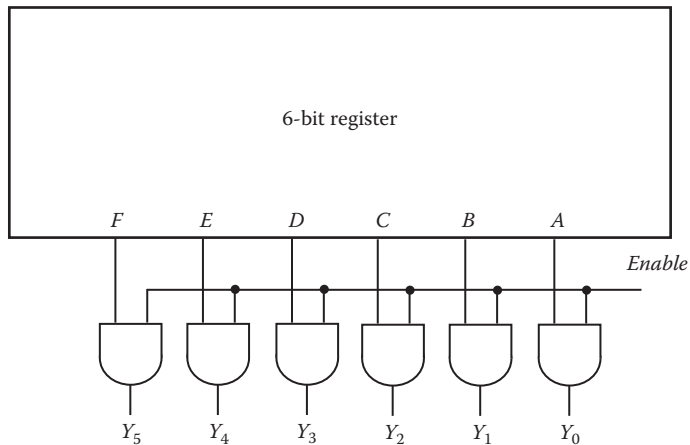



Figure 2.14  
Using AND gates to block or transmit data.

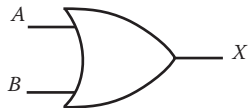

(a)

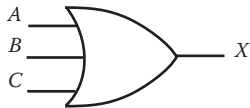


(b)

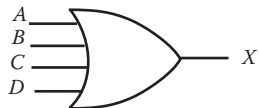


(c)


Figure 2.15  
OR gate symbols.

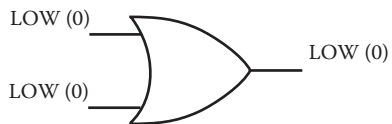


(a)

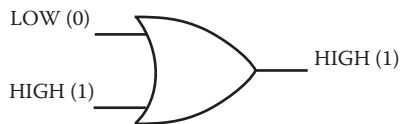

(b)

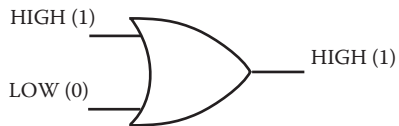

(c)

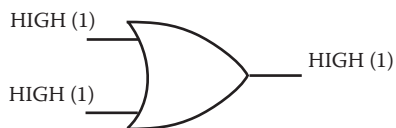

(d)

Figure 2.16  
Operation of a 2-input OR gate.



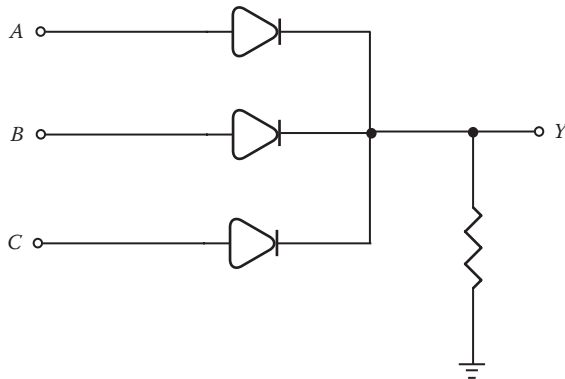


Figure 2.17  
A 3-input diode OR gate.

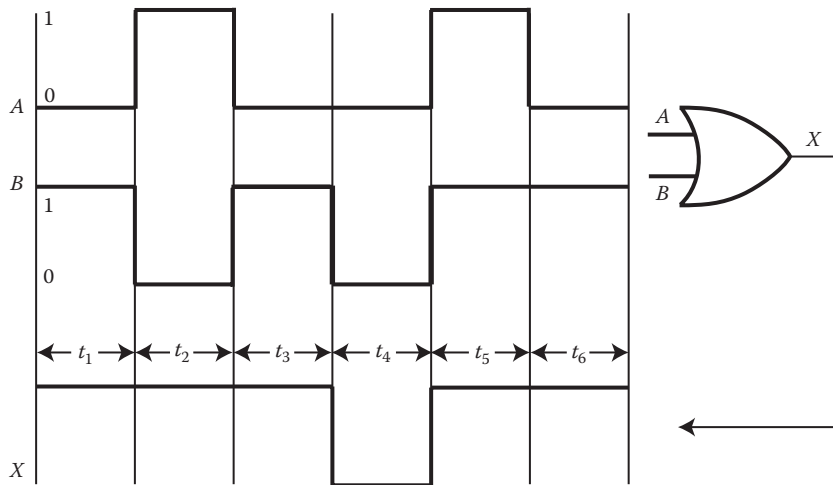


Figure 2.18  
Example of OR gate operation with a timing diagram showing input and output relationships.

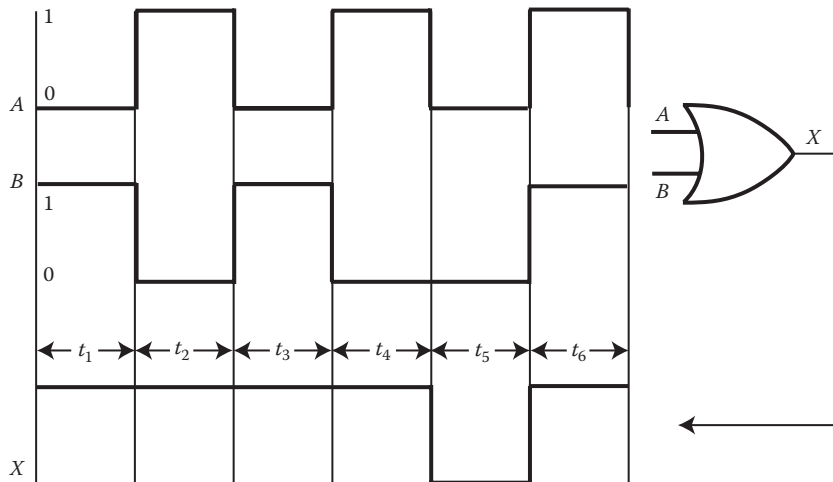


Figure 2.19  
Timing diagram with a 2-input OR gate.

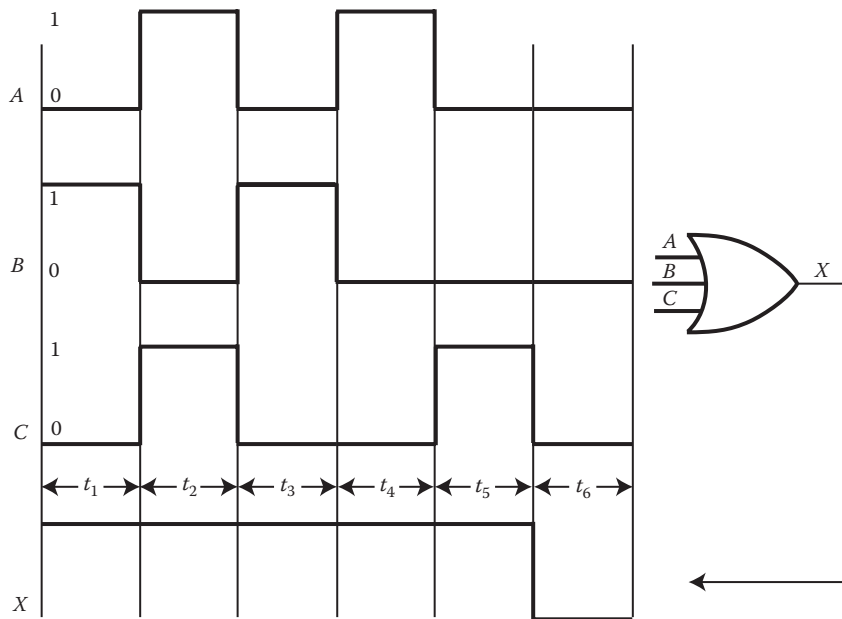


Figure 2.20  
Timing diagram with a 3-input OR gate.

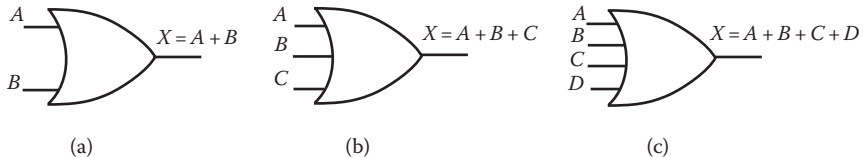


Figure 2.21  
Boolean expressions for OR gates with two, three, and four inputs.



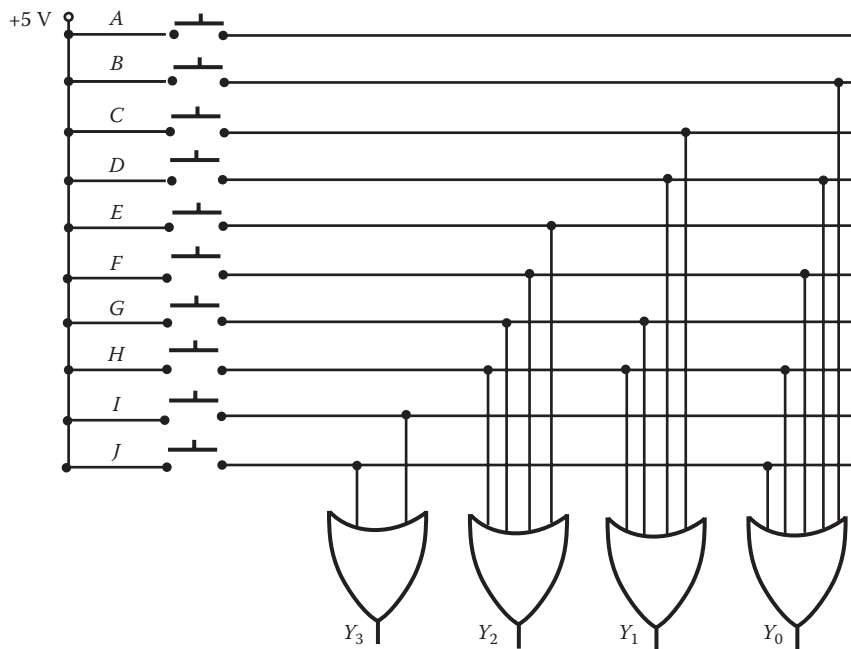



Figure 2.22  
Decimal-to-binary encoder.

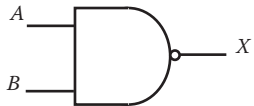

(a)

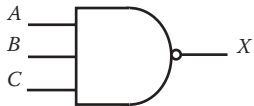

(b)

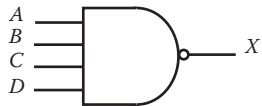

(c)

Figure 2.23  
NAND gate symbols.


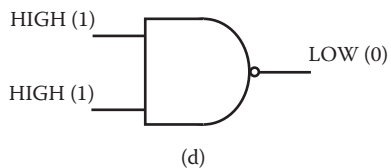
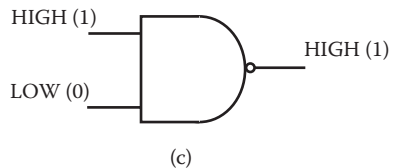
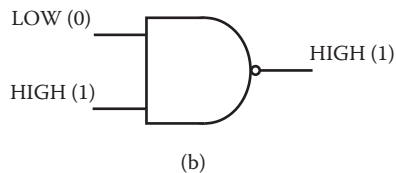


Figure 2.24  
Operation of a 2-input NAND gate.

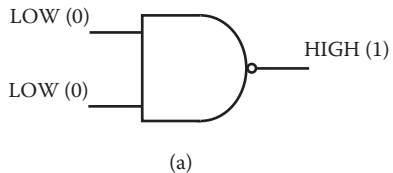

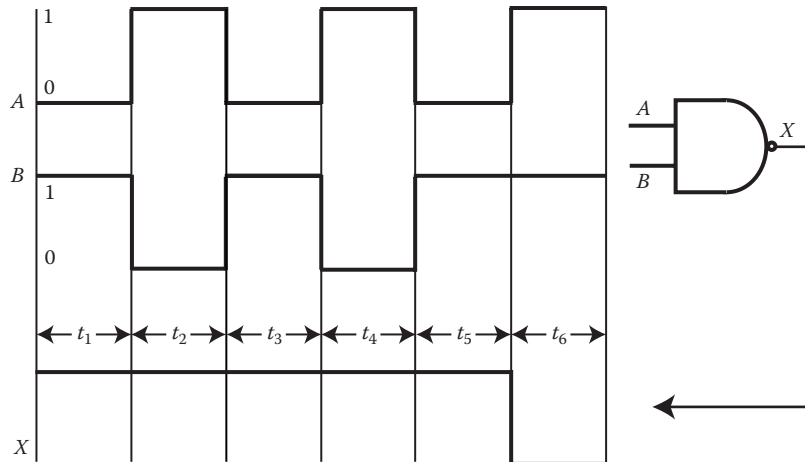


Figure 2.25  
Timing diagram for a 2-input NAND gate.



Figure 2.26

Standard symbols representing the two equivalent operations of a NAND gate.



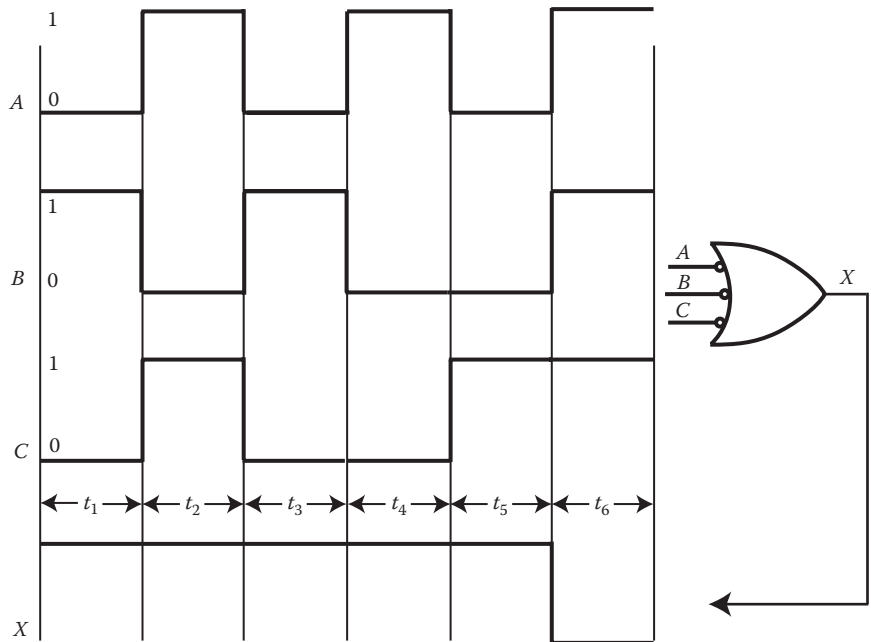



Figure 2.27  
Timing diagram for Example 2.11.

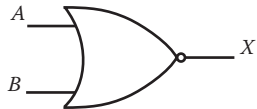

(a)

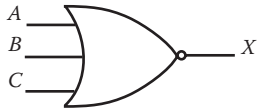

(b)

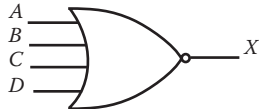

(c)

Figure 2.28  
NOR gate symbols.

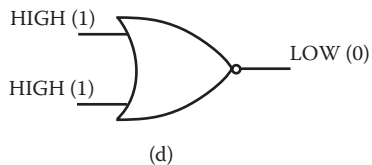
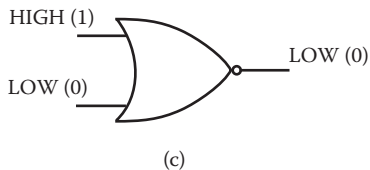
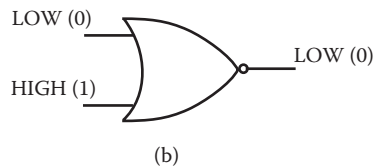
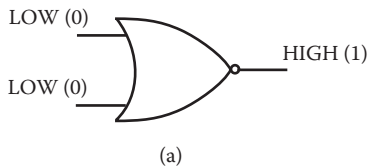


Figure 2.29  
Operation of a 2-input NOR gate.

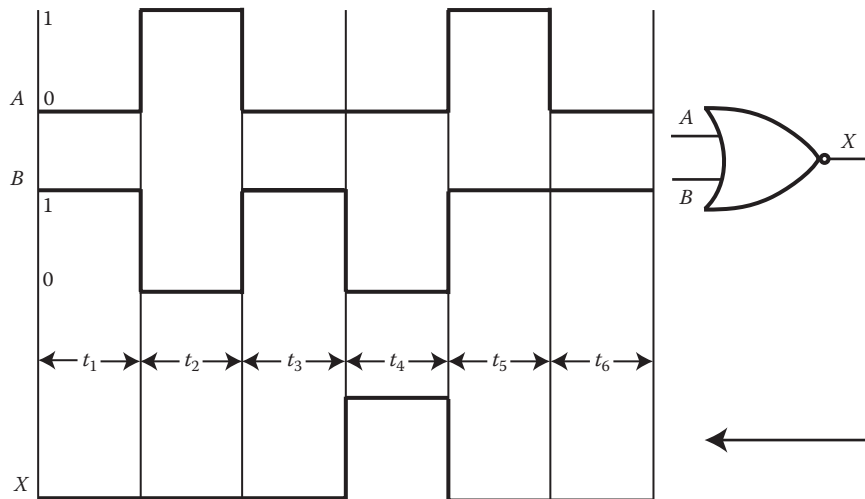


Figure 2.30  
Timing diagram for a 2-input NOR gate.

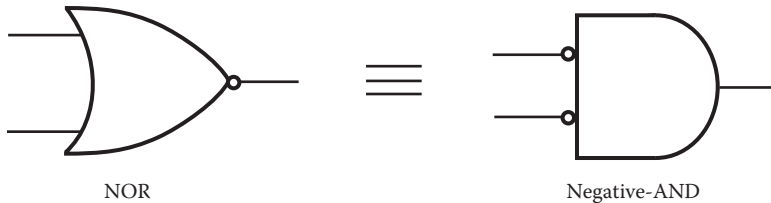


Figure 2.31  
Standard symbols representing the two equivalent operations of a NOT gate.



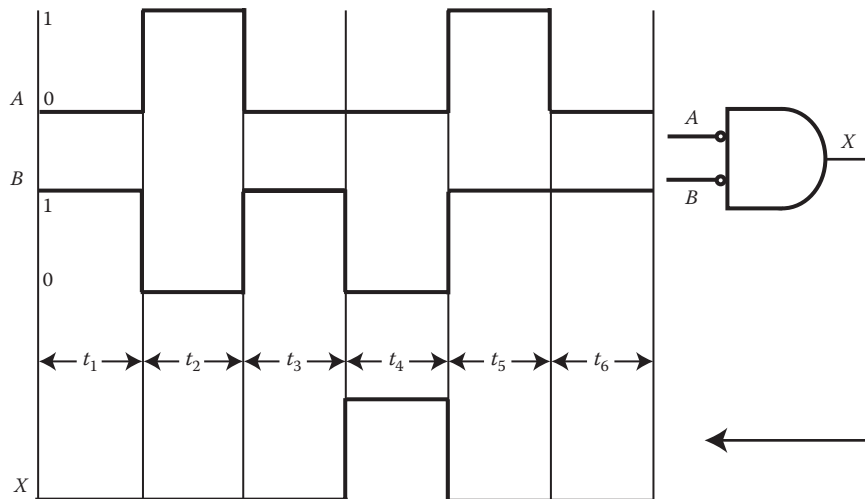


Figure 2.32  
Timing diagram for Example 2.14.

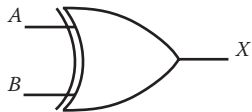

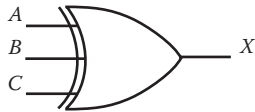

(a)



(b)



(c)

Figure 2.33  
XOR gate symbols.



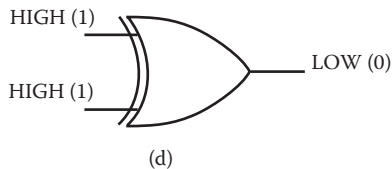
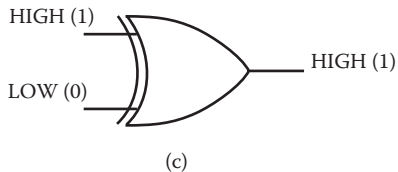
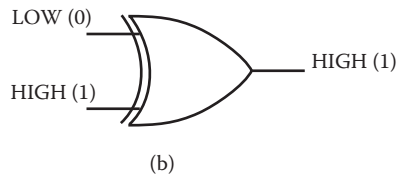


Figure 2.34  
Operation of XOR gate.

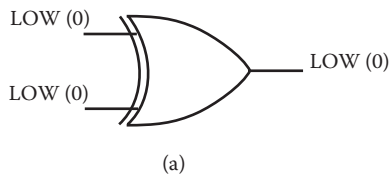

(a)

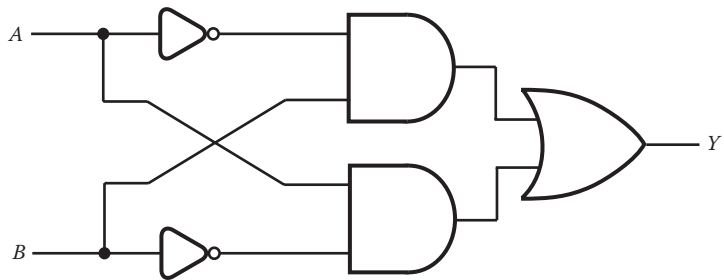

(b)

Figure 2.35  
(a) XOR gate, (b) a 2-input XOR gate.

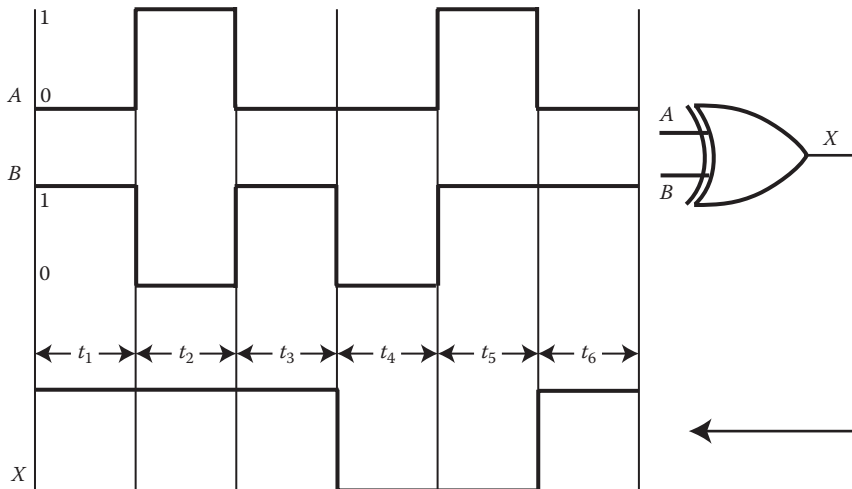


Figure 2.36  
Timing diagram for XOR gate.

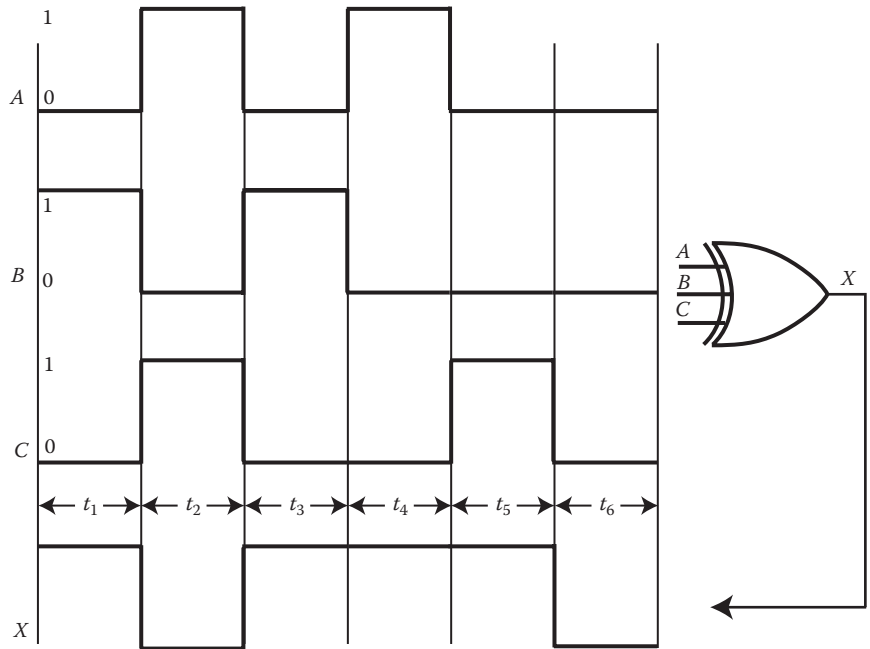


Figure 2.37  
Timing diagram for XOR gate.

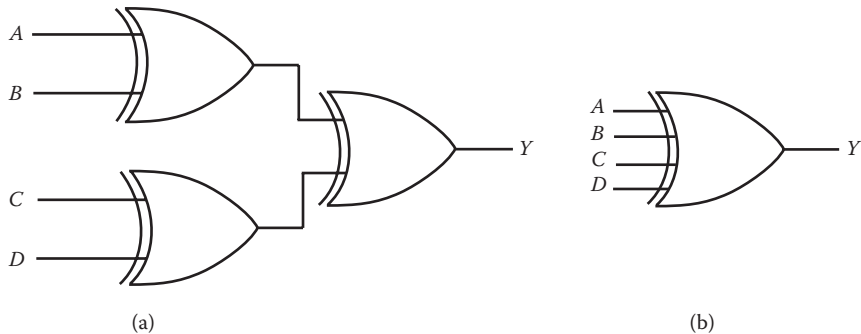


Figure 2.38

A 4-input XOR gate: (a) circuit with 2-input XOR gates, (b) equivalent logic symbol.



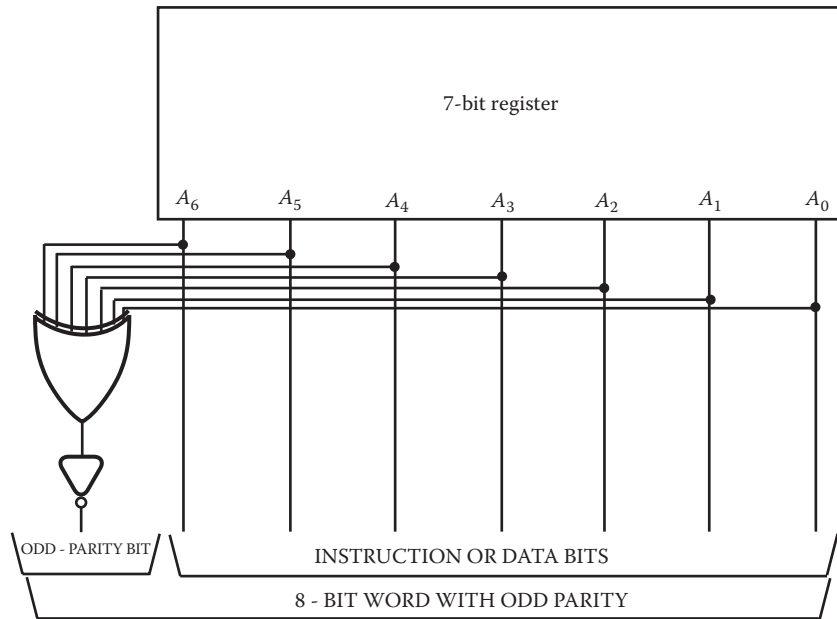



Figure 2.39  
Odd-parity generator.

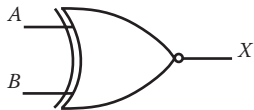

(a)

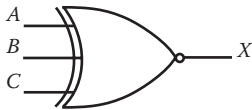


(b)

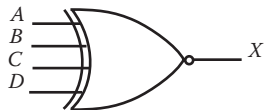


(c)

Figure 2.40  
XNOR gate symbols.




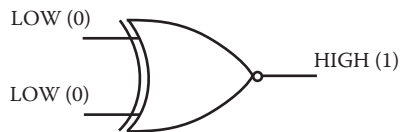


(a)

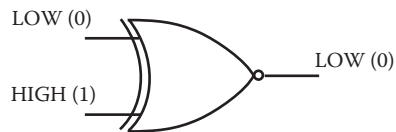

(b)

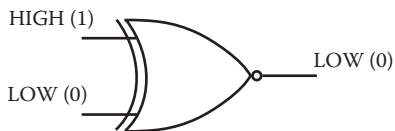

(c)

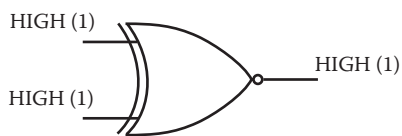

(d)

Figure 2.41  
Operation of XNOR gate.

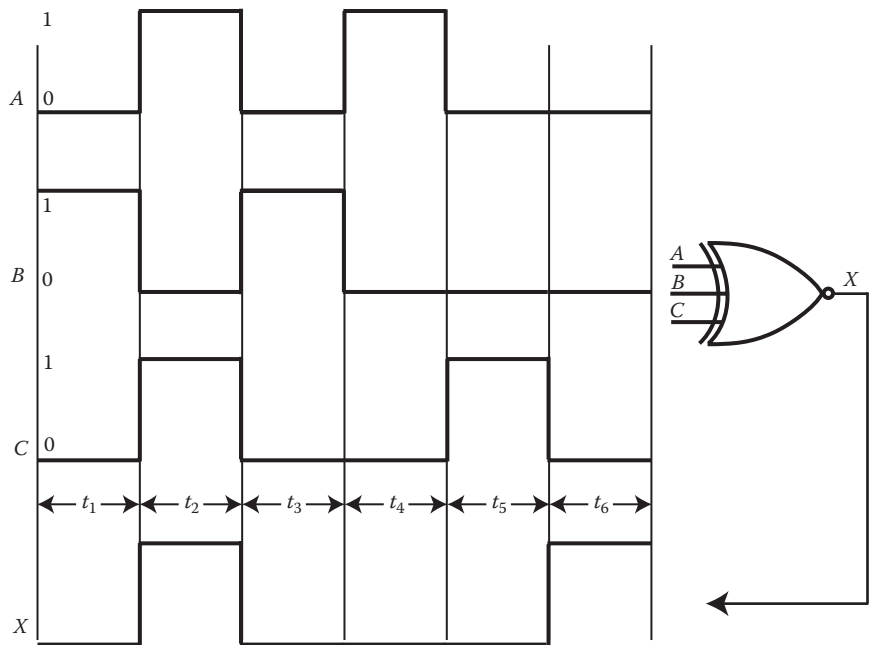


Figure 2.42  
Timing diagram for XNOR gate.

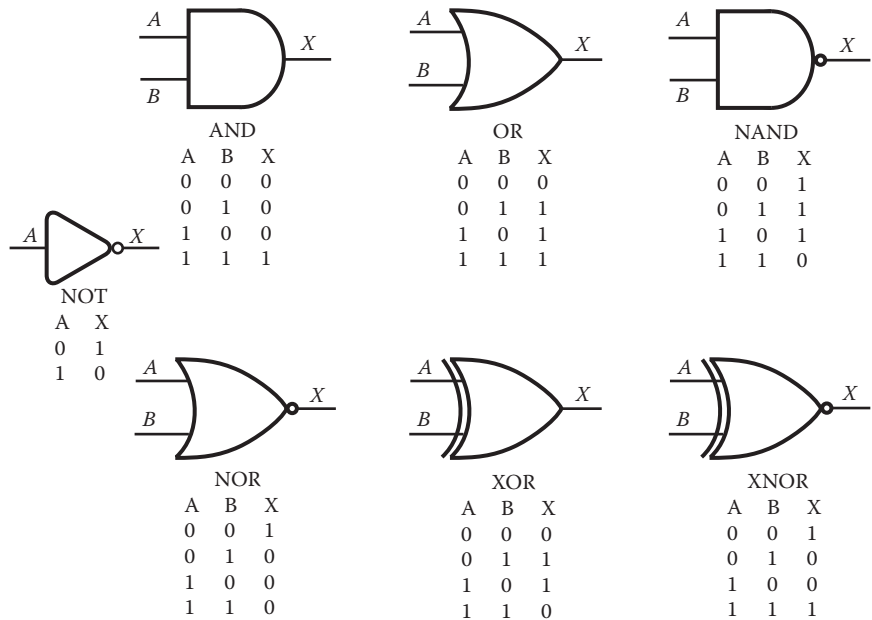


Figure 2.43  
Summary of major gates.

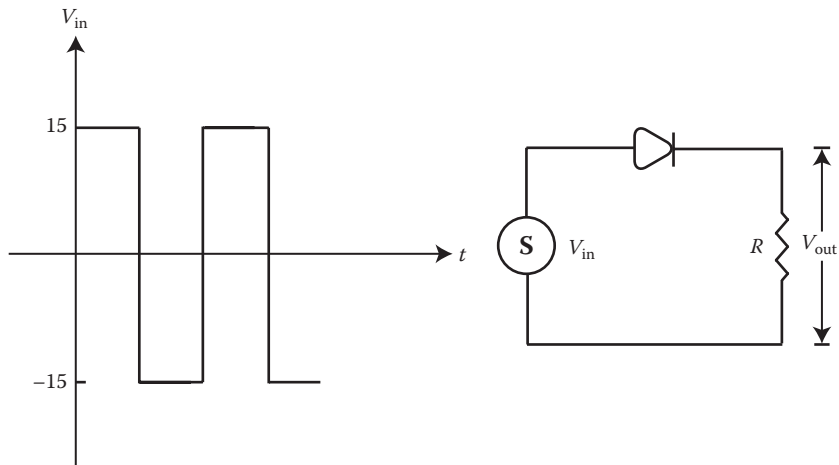


Figure 2.44  
Circuit diagram for Problem 2.1.

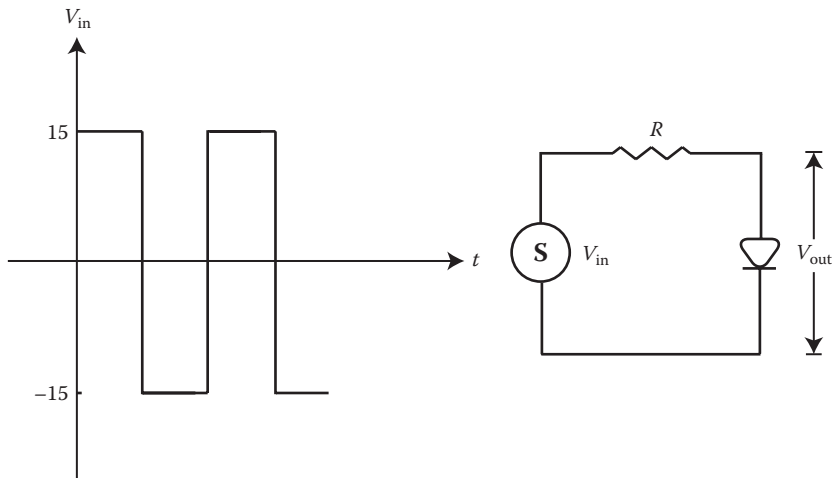


Figure 2.45  
Circuit diagram for Problem 2.2.

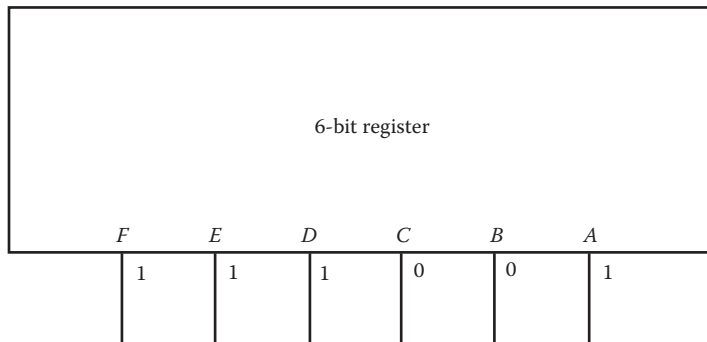


Figure 2.46  
Basic setup for Problem 2.3.

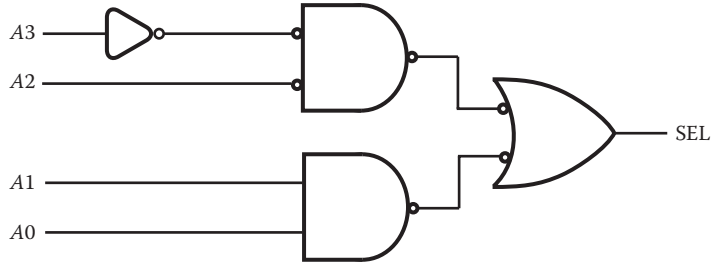


Figure 2.47  
Logic circuit for Problem 2.7.

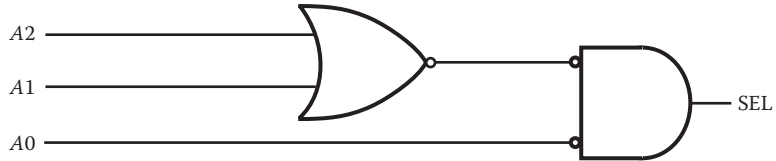


Figure 2.48  
Logic circuit for Problem 2.8.



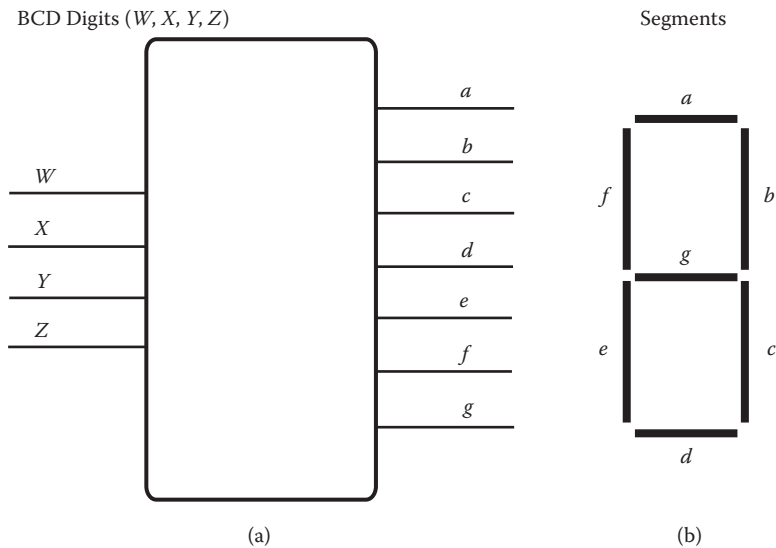


Figure 2.49  
Basic setup for Problem 2.9.

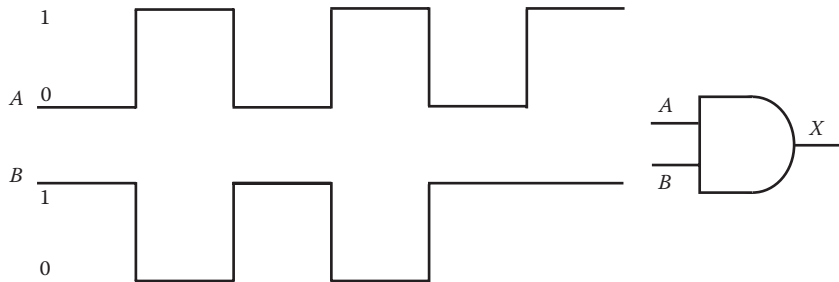


Figure 2.50  
Input signals for Problem 2.11.

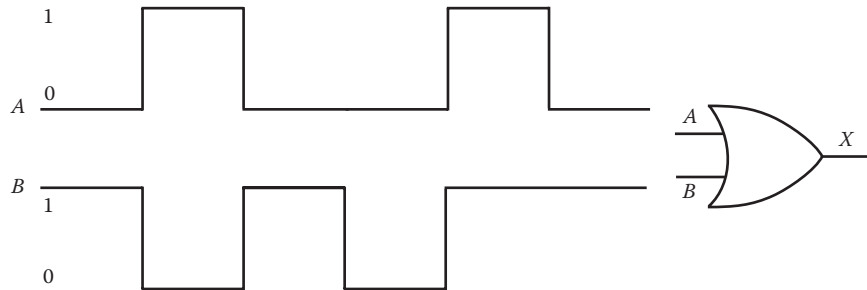


Figure 2.51  
Input signals for Problem 2.14.

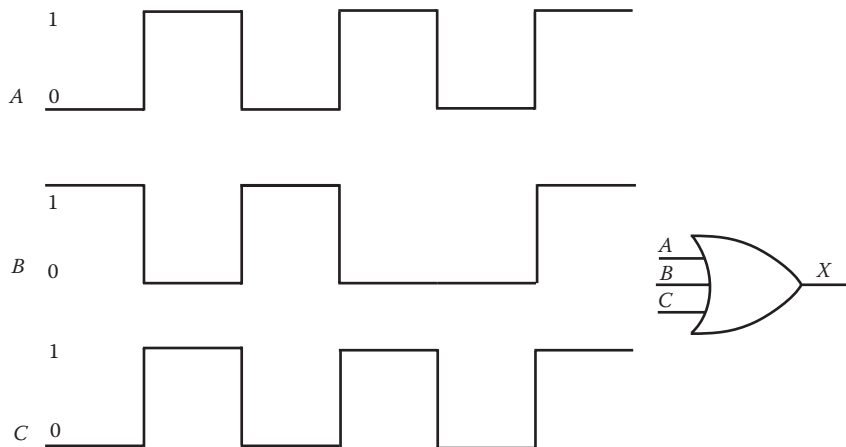


Figure 2.52  
Input signals for Problem 2.15.

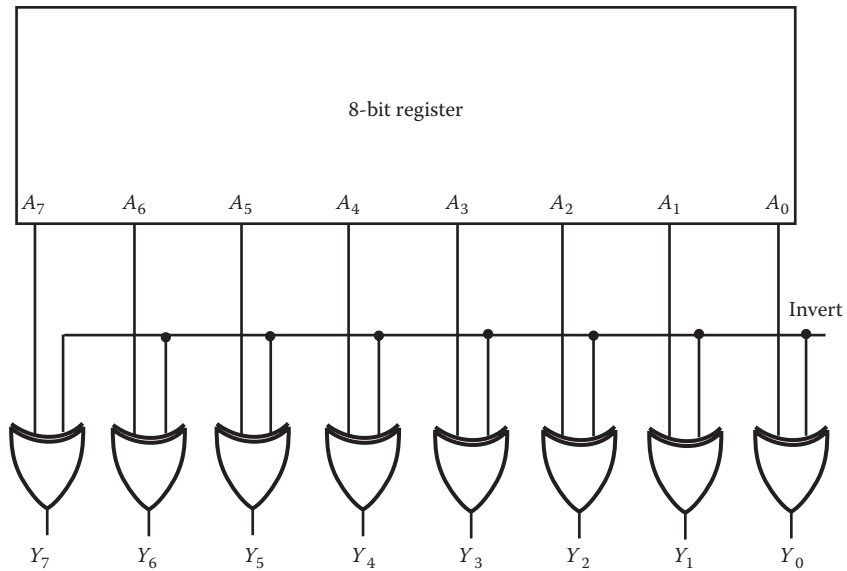


Figure 2.53  
A controlled inverter.