

4.1 Since the charging current due to the capacitance of a short line may be neglected,

$$I_S = I_R = I$$

Using I as the reference vector,

$$V_S = [(V_R \cos \phi_R + IR)^2 + (V_R \sin \phi_R \pm IX)^2]^{1/2}$$

$$\text{therefore, } \phi_S = \tan^{-1} \frac{V_R \sin \phi_R \pm IX}{V_R \cos \phi_R + IR}$$

The phasor diagram is shown below, in Figure P 2.12.

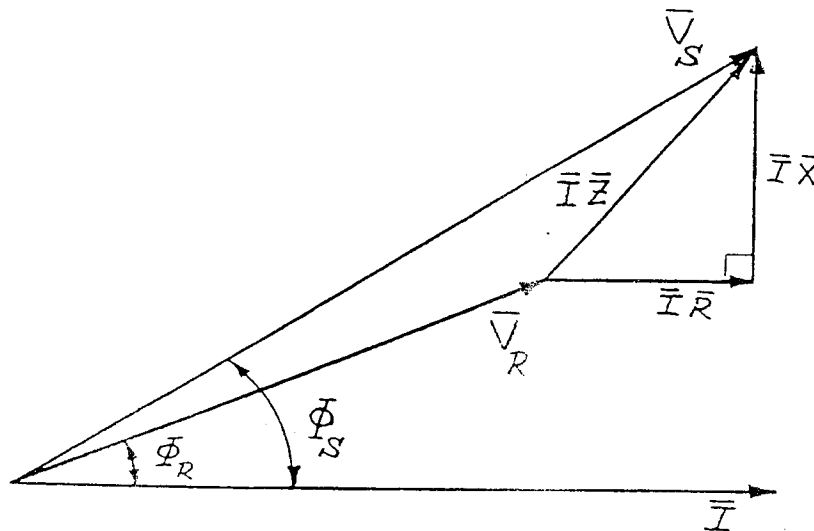


Figure P 2.12

4.2 From Table A.3, $X_a = 0.458 \, \Omega/\text{mi}/\phi$, or $X_a = 0.458 (15 \text{ mi}) = 6.87 \, \Omega/\phi$.

From Table A.8, for 3 ft separation, $X_d = 0.1333 \, \Omega/\text{mi}/\phi$, or $X_d = 1.9995 \, \Omega/\phi$. Therefore,

$$X_L = X_a + X_d = 6.87 + 1.9995 = 8.87 \Omega/\Phi$$

$$\text{Also, } R_a = 0.311 \Omega/\text{mi}/\Phi, \text{ or } R_a = 4.665 \Omega/\Phi$$

$$\text{Thus, } Z_L = 4.665 + j8.87 \Omega/\Phi$$

$$I_L = \frac{P_{3\Phi}}{\sqrt{3} V_{L-L} \cos\Phi} = \frac{10 \times 10^6}{\sqrt{3} (34.5 \times 10^3) 0.9} = 185.942 \text{ A}$$

$$\text{or } \bar{I}_L = 185.942 / -25.84^\circ \text{ A}$$

Therefore,

$$\begin{aligned} \bar{V}_{S(L-N)} &= \bar{V}_{R(L-N)} + \bar{I}_L \bar{Z}_L \\ &= 19,917 / 0^\circ + (185.942 / -25.84^\circ)(4.665 + j8.87) \\ &= 21,414 + j1103.9 = 21.442 / 2.95^\circ \text{ kV} \end{aligned}$$

$$\text{or } \bar{V}_{S(L-L)} = \sqrt{3}(21.442 / 2.95^\circ + 30^\circ) = 37.149 / 32.95^\circ \text{ kV}$$

$$(b) \cos\Phi_S = \cos[\theta_{\bar{V}_S} - \theta_{\bar{I}_S}] = \cos[2.95 - (-25.84)]$$

$$= \cos 28.74^\circ = 0.876 \text{ lagging.}$$

(c) The transmission efficiency is

$$\eta = \frac{\text{Output}}{\text{Input}} 100 = \frac{\sqrt{3} V_{R(L-L)} I_R \cos\theta_R}{\sqrt{3} V_{S(L-L)} I_S \cos\theta_S} 100$$

$$\eta = \frac{V_{R(L-L)} \cos\theta_R}{V_{S(L-L)} \cos\theta_S} 100 = \frac{(19.919) 0.9}{(21.442) 0.8768} 100 = 95.4\%$$

$$(d) \% \text{VReg.} = \frac{|V_S| - |V_R|}{|V_R|} 100 = \frac{21.442 - 19.919}{19.919} 100 = 7.66\%$$

4.3 (a) From Table A.3, $X_a = 0.458 \Omega/\text{mi}/\Phi$, or

$$X_a = 0.458 (15 \text{ mi}) = 6.87 \Omega/\Phi$$

From Table A.8, for 3 ft separation,

$$X_d = 0.1333 \Omega/\text{mi}/\Phi, \text{ or } X_d = 1.9995 \Omega/\Phi$$

Therefore,

$$X_L = X_a + X_b = 6.87 + 1.9995 = 8.8695 \Omega/\Phi$$

$$\text{Also, } R_a = 0.311 \Omega/\text{mi}/\Phi, \text{ or } R_a = 4.665 \Omega/\Phi$$

$$\text{Thus, } Z_L = 4.665 + j8.8695 \Omega/\Phi$$

$$I_L = \frac{10 \times 10^6}{\sqrt{3}(34.5 \times 10^3)0.8} = 209.1849$$

$$\text{or } \bar{I}_L = 209.1849 / -36.87^\circ \text{ A}$$

$$\bar{V}_S = \bar{V}_R + \bar{I}_L \bar{Z}_L = 21,812.443 + j898.8652$$

$$= 21,830.9557 / 2.36^\circ \text{ V}$$

$$\text{or } \bar{V}_{S(L-L)} = \sqrt{3}(21,830.9557 / 2.36^\circ + 30^\circ)$$

$$= 37,812.3856 / 32.36^\circ \text{ V}$$

$$(b) \cos \phi_S = \cos[\theta_{\bar{V}_S} - \theta_{\bar{I}_S}] = \cos[2.36^\circ - (-36.87^\circ)]$$

$$= 0.7746 \text{ lagging}$$

$$(c) \eta = \frac{19,918.5843 \times 0.8}{21,830.9557 \times 0.7746} 100 = 94.23\%$$

$$(d) \% \text{VReg} = \frac{\frac{|V_{S(N-L)}| - |V_{R(F-L)}|}{|V_{R(F-L)}|} 100}{100}$$

$$= \frac{21,830.9557 - 19,918.5843}{19,918.5843} 100 = 9.6\%$$

4.4 (a) $\bar{I}_L = 209.1849/\underline{36.87}^\circ \text{ A}$

$$\bar{V}_S = \bar{V}_R + \bar{I}_L \bar{Z}_L = 19,695.1012/\underline{6.03}^\circ \text{ V}$$

$$\begin{aligned} \text{or } \bar{V}_{S(L-L)} &= \sqrt{3} \bar{V}_{S(L-N)} = 34,112.9159/\underline{6.03}^\circ + 30^\circ \\ &= 34,112.9159/\underline{36.03}^\circ \text{ V} \end{aligned}$$

$$\begin{aligned} \text{(b) } \cos\phi_S &= \cos[\phi_{\bar{V}_S} - \phi_{\bar{I}_S}] \\ &= \cos[6.03 - 36.87] = \cos[-30.84] = 0.86 \text{ leading} \end{aligned}$$

$$\text{(c) } = \frac{(34.5 \times 10^3)(0.8)}{34,112.9159 \times 0.86} = 94.23\%$$

$$\text{(d) } \%V_{\text{Reg}} = \frac{19,695 - 19,918}{19,918} 100 = -1.12\%$$

Note that the voltage rise is due to the Ferranti Effect. The circuit provides for the absorption of reactive power by the series impedance I^2X , but does not provide for its supply by the shunt admittance V^2B which becomes more important as the voltage is increased, and therefore does not take into account the increase of the receiving-end voltage on light load. For longer lines at higher voltages, this voltage rise will be considerably greater. On the other hand, quite a small load is sufficient to eliminate the Ferranti Effect. Therefore, when a long line is terminated in a transformer, the magnetizing current is often enough to eliminate V_R becoming greater than V_S .

4.5 The load is connected to the secondary-side of the transformer that is supplied by the feeder. Thus, the transformer is connected to the receiving-end of the feeder. Since the load voltage is $V_{L(LV)} = 2250$ V or referred to the high-voltage (i.e., primary) side of the transformer,

$$V_{L(HV)} = 2250 \left(\frac{19,900}{2,400} \right) = 18,656.25 \text{ V}$$

with $\cos\theta_L = 0.85$ leading

$$\text{thus, } S_L = \frac{200 \times 10^3}{0.85} = 235,294.12 \text{ VA}$$

Therefore, the load current at the primary-side of the transformer is

$$I_{L(HV)} = \frac{235,294.12}{18,656.25} = 12.6121 \text{ A}$$

The transformer impedance referred to the primary side of the transformer is

$$\bar{Z}_{T(HV)} = (0.24 + j0.99) \left(\frac{19,900}{2,400} \right)^2 = 16.5 + j68.0642 \text{ } \Omega$$

$$\text{Thus, } \bar{Z}_{eq} = \bar{Z}_{feeder} + \bar{Z}_{T(HV)}$$

$$= (95 + j340) + (16.5 + j68.0642)$$

$$= 111.5 + j408.0642 = 423.0232 / \underline{74.72}^\circ \text{ } \Omega$$

(a) Taking $I_{L(HV)}$ as reference,

$$\bar{V}_{S(L-N)} = \bar{V}_{R(L-N)} + \bar{I}_{L(HV)} \bar{Z}_{eq}$$

$$\text{where } \bar{V}_{R(L-N)} = \bar{V}_{L(HV)} = 18,656.25 / \underline{-31.79}^\circ \text{ V}$$

$$\begin{aligned}
 \text{thus, } \bar{V}_{S(L-N)} &= 18,656.25(0.85 - j0.5268) \\
 &\quad + (12.6121/\underline{0^\circ})(423.0232/\underline{74.72^\circ}) \\
 &= 17,263.8345 - j4,681.5041 \\
 &= 17,887.3269/\underline{-15.17^\circ} \text{ V}
 \end{aligned}$$

$$\begin{aligned}
 \text{(b) } \bar{V}_{T(HV)} &= \bar{V}_{L(HV)} + \bar{I}_{L(HV)} \bar{Z}_{T(HV)} \\
 &= 18,656.25/\underline{-31.79^\circ} + (12.6121/\underline{0^\circ})(70.0356/\underline{76.37^\circ}) \\
 &= 16,065.9126 - j8,969.6801 \\
 &= 18,400.2367/\underline{-29.17^\circ} \text{ V}
 \end{aligned}$$

$$\begin{aligned}
 \text{(c) } P_S &= P_L + (P_{\text{loss in feeder and transformer}}) \\
 &= 200 \times 10^3 + 17,735.75 = 217,735.75 \text{ W}
 \end{aligned}$$

$$\text{where } P_{\text{loss}} = I_{L(HV)}^2 R_{\text{eq}}$$

$$Q_S = Q_L + I_{L(HV)}^2 X_{\text{eq}}$$

$$= -123,948.87 + 64,908.76 = -59,040.11 \text{ vars}$$

Alternatively,

$$\begin{aligned}
 \bar{S}_S &= \bar{V}_{S(L-N)} \bar{I}_{L(HV)}^* \\
 &= (17,887.3269/\underline{-15.17^\circ})(12.6121/\underline{0^\circ}) \\
 &= 217,735.53 - j59,035.03 \text{ VA}
 \end{aligned}$$

Checks!

$$\underline{4.6} \quad (a) \quad \bar{I}^* = \frac{\bar{S}_R}{\bar{V}_R} = \frac{(15 + j12) \times 10^6}{(115 + j0) \times 10^3} = 167.04 / \underline{38.66}^\circ \text{ A}$$

$$\begin{aligned} \text{thus, } \bar{V}_S &= \bar{V}_R + \bar{I}_R \bar{Z}_L = (115 + j0) \times 10^3 + (167.04 / \underline{-38.66}^\circ) 15 / \underline{90}^\circ \\ &= 116,565.24 + j1,956.54 = 116,581.3 / \underline{0.96}^\circ \text{ V} \end{aligned}$$

$$(b) \quad \bar{I}_S = \bar{I}_R = 167.04 / \underline{-38.66}^\circ \text{ A}$$

$$\begin{aligned} \underline{4.7} \quad (a) \quad \bar{V}_{S(L-N)} &= \bar{V}_{R(L-N)} + \bar{I}_R \bar{Z}_L \\ &= 39,837.2 / \underline{0}^\circ + (300 / \underline{-30}^\circ) (44.94 / \underline{57.7}^\circ) \\ &= 52,150.17 / \underline{6.9}^\circ \text{ V} \end{aligned}$$

$$\%V_{\text{Reg}} = \frac{\frac{|\bar{V}_S| - |\bar{V}_R|}{|\bar{V}_R|}}{1} 100 = \frac{52,150.17 - 39,837.2}{39,837.2} 100 = 30.9\%$$

$$(b) \quad \begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} 1 & 44.94 / \underline{57.72}^\circ \\ 0 & 1 \end{bmatrix}$$

(c) The phasor diagram is shown below, in Figure P2.18.

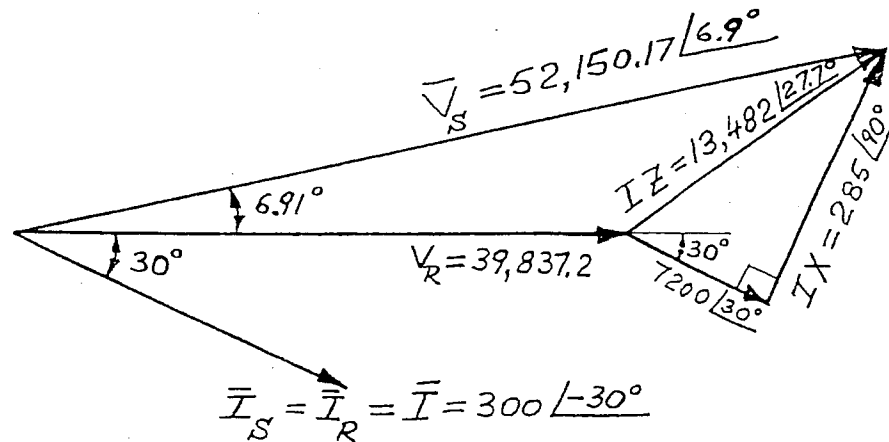


Figure P2.18

4.8 (a) $\bar{I}_R = 300 \angle -45^\circ = 212.1 - j212.1 \text{ A}$

$$\bar{V}_S = \bar{V}_R + \bar{I}_R \bar{Z} = 39,837.17 + (300 \angle -45^\circ)(44.94 \angle 57.7^\circ)$$

$$= 52,989.58 + j2,968.85 = 53,072.6 \angle 3.2^\circ \text{ V}/\phi$$

$$\%VR_{eg} = \frac{\frac{|\bar{V}_S| - |\bar{V}_R|}{|\bar{V}_R|}}{1} 100 = \frac{53,072.6 - 39,837.17}{39,837.17} 100 = 33.22\%$$

$$(b) \begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} 1 & Z \\ 0 & 1 \end{bmatrix} = \begin{bmatrix} 1 & 44.94 \angle 57.7^\circ \\ 0 & 1 \end{bmatrix}$$

(c) The phasor diagram is shown below, in Figure P2.19

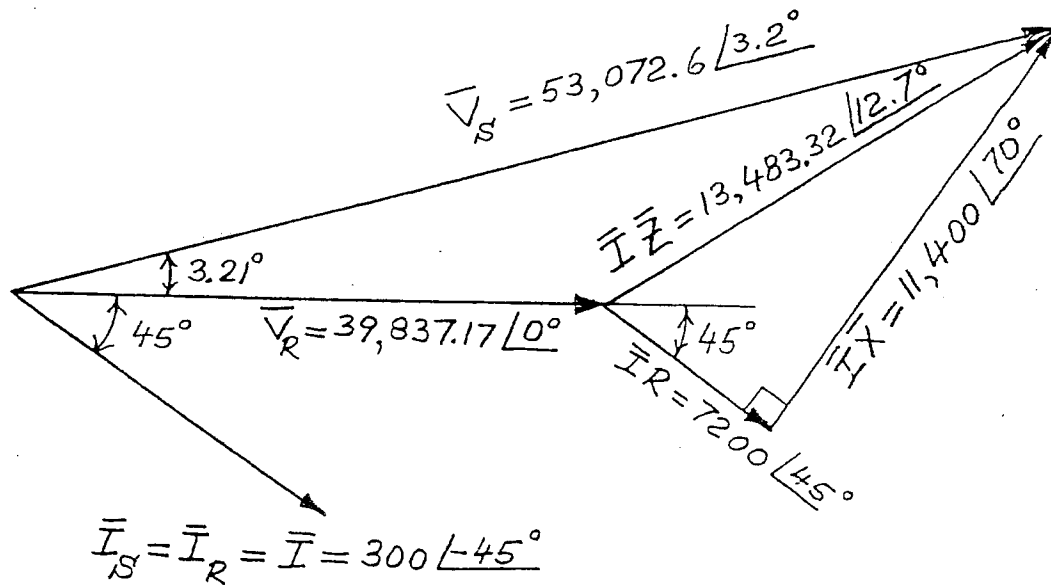


Figure P2.19

4.9 (a)

$$I_L = \frac{P_{3\phi}}{\sqrt{3} V_L \cos \phi} = \frac{12 \times 10^6}{\sqrt{3} (138 \times 10^3) 0.85} = 59.06 \text{ A}$$

$$\bar{I} = 59.06(0.85 - j0.527) = 50.2044 - j31.1246 = 59.06 / -31.8^\circ$$

$$R = r \cdot \ell = 4 \times 40 = 160 \Omega / \phi$$

$$X_L = x_a \cdot \ell = 2\pi 60 (14 \times 10^{-3}) 40 = 211.112 \Omega / \phi$$

$$Z_L = R + jX_L = 160 + j211.112 \Omega / \phi$$

$$\bar{V}_{R(L-N)} = \frac{138 \times 10^3 / 0^\circ}{\sqrt{3}} = 79,674.3 / 0^\circ \text{ V}$$

$$\bar{V}_{S(L-N)} = \bar{V}_{R(L-N)} + \bar{I}_R \bar{Z}_L = 94,445.54 / 3.4^\circ \text{ V}/\phi$$

$$|V_{S(L-L)}| = \sqrt{3} V_{S(L-N)} = 163,584.47 \text{ V}$$

$$(b) \quad P_{\text{LOSS}} = 3I_R^2 R = 3(59.06)^2 160 = 1.67 \text{ MW}$$

$$\text{thus, } P_S = P_R + P_{\text{LOSS}} = 12 + 1.67 = 13.67 \text{ MW}$$

$$\text{or } P_{3\phi(\text{LOSS})} = P_{3\phi(\text{in})} - P_{3\phi(\text{out})}$$

$$= \sqrt{3} V_{S(L-L)} I_L \cos(\theta_{\bar{V}_S} - \theta_{\bar{I}}) - 12 \times 10^6$$

$$= \sqrt{3} (163,584.47)(59.06) \cos(3.4^\circ + 31.8^\circ)$$

$$\approx 1.67 \text{ MW}$$

$$(c) \quad I_L = \frac{P_{3\phi}}{\sqrt{3} V_{R(L-L)} \cos \theta_R} = \frac{12 \times 10^6}{\sqrt{3} (138 \times 10^3) \times 1.0} = 50.2044 \text{ A}$$

$$P_{L(\text{new})} = P_{3\phi(\text{LOSS})} = 3I_R^2 R = 3(50.2044)^2 160 = 1.208 \text{ MW}$$

$$\text{Reduction in } P_{\text{LOSS}} = P_{L(\text{old})} - P_{L(\text{new})}$$

$$= 1.67 - 1.208 = 0.462 \text{ MW}$$

$$\underline{4.10} \quad \bar{Z} = 18 + j57 = 59.7746 / 72.47^\circ \Omega$$

$$\text{From Eq. (2.180), } P_{R,\text{max}} = \frac{V_R^2}{Z^2} \left(\frac{V_S \cdot Z}{V_R} - R \right)$$

where

$$V_{R(L-N)} = \frac{34.5 \times 10^3}{\sqrt{3}} = 19,918.6 \text{ V}$$

$$V_{S(L-N)} = \frac{39 \times 10^3}{\sqrt{3}} = 22,516.6 \text{ V}$$

Thus,

$$\begin{aligned} P_{R, \max} &= \frac{19,918.6^2}{59.7746^2} \left(\frac{22,516.6 \times 59.7746}{19,918.6} - 18 \right) \\ &= 5.504 \text{ MW} \end{aligned}$$

4.11 (a) From Tables A.1 and A.8,

$$Z_1 = [r_a + j(x_a + x_d)] \ell$$

$$= [0.303 + j(0.497 + 0.1682)]45 = 32.8931/\underline{65.5^\circ} \Omega$$

$$I_R = \frac{20 \times 10^6}{\sqrt{3} (161 \times 10^3)} = 71.72 \text{ A or } \bar{I}_R = 71.72/\underline{-31.8^\circ} \text{ A}$$

$$\bar{V}_{S(L-N)} = \bar{V}_{R(L-N)} + \bar{I} \bar{Z}$$

$$= 92.9534 \times 10^3 / \underline{0^\circ} + (71.72 / \underline{-31.8^\circ})(32.8931 / \underline{65.5^\circ})$$

$$= 94,915.83 + j1,309.27 = 94,924.86 / \underline{0.8^\circ} \text{ V}$$

$$\% \text{VReg} = \frac{\frac{|\bar{V}_S| - |\bar{V}_R|}{|\bar{V}_R|}}{\frac{|\bar{V}_R|}{|\bar{V}_R|}} 100 = \frac{94,925 - 92,953}{92,953} 100 = 2.12\%$$

$$(b) \cos \phi_S = \cos(\theta_{\bar{V}_S} - \theta_{\bar{I}_S}) = \cos(0.8^\circ - (-31.8^\circ)) = 0.8426$$

(c) If the line is 1 ϕ ,

$$\eta = \frac{V_R I \cos \phi_R}{V_R I \cos \phi_R + 2 I^2 R} \times 100$$

$$= \frac{92,953 \times 71.72 \times 0.85}{92,953 \times 71.72 \times 0.85 + 2 \times 71.72^2 \times 13.635} 100$$

$$= 97.572\%$$

(d) If the line is 3ϕ ,

$$\eta = \frac{\sqrt{3} V_R I \cos \phi_R}{\sqrt{3} V_R I \cos \phi_R + 3 I^2 R} 100$$

$$= \frac{\sqrt{3} \times 92,953.4 \times 71.72}{\sqrt{3} \times 92,953.4 \times 71.72 \times 0.85 + 3 \times 71.72^2 \times 13.635} 100 = 97.89\%$$

4.12 $z_1 = 0.7 + j1.2 \Omega/\phi/\text{mi}$

$$Z_1 = (0.7 + j1.2)10 = 7 + j12 = 13.8924/59.7^\circ \Omega/\phi$$

$$V_S = \frac{71 \times 10^3}{\sqrt{3}} = 40,991.9 \text{ V}$$

$$V_R = \frac{69 \times 10^3}{\sqrt{3}} = 39,837.2 \text{ V}$$

$$V_{D_{\text{line}}} = 40,991.9 - 39,837.2 = 1154.73 = IZ_{\text{eq}}$$

$$\text{where } I = \frac{15 \times 10^6}{\sqrt{3} (69 \times 10^3) 0.9} = 139.456 \text{ A}$$

$$Z_{\text{eq}} = \frac{IZ_{\text{eq}}}{I} = \frac{1154.73}{139.456} = 8.28 \Omega$$

$$P_S = \frac{15 \times 10^6}{0.98} = 15,306,122.5 \text{ W}$$

$$P_{\text{LOSS}} = 3I^2 R = 306,122.5 \text{ W}$$

Therefore, the equivalent resistance of the two lines in parallel is

$$3I^2 R_{eq} = 306,122.5$$

$$R_{eq} = \frac{306,122.5}{3 \times 139.456^2} = 5.25 \Omega$$

$$\text{Thus, } X_{eq} = (Z_{eq}^2 - R_{eq}^2)^{1/2} = (8.28^2 - 5.25^2)^{1/2} = 1.74 \Omega$$

$$Z_{eq} = 5.25 + j1.74 = 5.5308/\underline{18.3}^\circ \Omega$$

$$\text{Since } Z_1 = 7 + j12 \Omega \text{ and } \frac{1}{Z_{eq}} = \frac{1}{Z_1} + \frac{1}{Z_2}$$

$$Z_2 = \frac{Z_1 \cdot Z_{eq}}{Z_1 - Z_{eq}}$$

$$\text{where } Z_1 - Z_{eq} = (7 + j12) - (5.25 + j1.74) = 1.75 + j10.26$$

Therefore,

$$Z_2 = \frac{(7 + j12)(5.25 + j1.74)}{(7 + j12) - (5.25 + j1.74)} = 7.3766 - j0.2885 = 7.3923/\underline{-2.4}^\circ$$

$$\text{That is, } R_2 = 7.366 \Omega \text{ and } X_2 = 0.2885/\underline{-90}^\circ \Omega$$

$$\begin{aligned} \underline{4.13} \quad \frac{\cosh y\ell - 1}{\sinh y\ell} &= \frac{\cosh y\ell - (\cosh^2 y\ell - \sinh^2 y\ell)}{\sinh y\ell} \\ &= \frac{\frac{1}{2}(e^{y\ell} - e^{-y\ell}) - [\frac{1}{2}(e^{y\ell} - e^{-y\ell})]^2 + [\frac{1}{2}(e^{y\ell} - e^{-y\ell})]^2}{\frac{1}{2}(e^{y\ell} - e^{-y\ell})} \\ &= \frac{e^{y\ell} + e^{-y\ell} - 2e^{-y\ell}y\ell}{e^{y\ell} - e^{-y\ell}} \\ &= \frac{(e^{y\ell/2} - e^{-y\ell/2})^2}{(e^{y\ell/2} - e^{-y\ell/2})(e^{y\ell/2} + e^{-y\ell/2})} \\ &= \frac{e^{y\ell/2} - e^{-y\ell/2}}{e^{y\ell/2} + e^{-y\ell/2}} = \tanh \frac{1}{2}y\ell \end{aligned}$$

4.14 Left to the reader.

4.15 Considering the network as a series connection of single two-port elements,

$$\begin{aligned}
 \begin{bmatrix} A & B \\ C & D \end{bmatrix} &= \begin{bmatrix} 1 & j4 \\ 0 & 1 \end{bmatrix} \begin{bmatrix} 0 & 0 \\ 0.04 & 1 \end{bmatrix} \begin{bmatrix} 1 & 6 \\ 0 & 1 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ j0.02 & 1 \end{bmatrix} \begin{bmatrix} 1 & j5 \\ 0 & 1 \end{bmatrix} \\
 &= \begin{bmatrix} 0.9433/\underline{17.3}^\circ & 10.5226/\underline{64.1}^\circ \\ 0.0471/\underline{31.8}^\circ & 1.1338/\underline{10.2}^\circ \end{bmatrix} \\
 &= \begin{bmatrix} 0.9008 + j0.28 & 4.6 + j9.464 \\ 0.04 + j0.0248 & 1.116 + j0.2 \end{bmatrix}
 \end{aligned}$$

Alternatively, the network can be considered as the series connection of a π -network (made up of Y_1 , Z_2 , and Y_2 elements) with the elements Z_1 and Z_3 . Therefore,

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} A_1 & B_1 \\ C_1 & D_1 \end{bmatrix} \begin{bmatrix} A_2 & B_2 \\ C_2 & D_2 \end{bmatrix} \begin{bmatrix} A_3 & B_3 \\ C_3 & D_3 \end{bmatrix}$$

$$= \begin{bmatrix} 1 & j4 \\ 0 & 1 \end{bmatrix} \begin{bmatrix} 1+ZY_2 & Z \\ Y_1+Y_2+ZY_1Y_2 & 1+ZY_1 \end{bmatrix} \begin{bmatrix} 1 & j5 \\ 0 & 1 \end{bmatrix}$$

The answer turns out to be the same.

$$\begin{aligned} \underline{4.16} \quad Z_1 &= \frac{A-1}{C} = \frac{(0.9008 + j0.28) - 1}{0.04 + j0.0248} = \frac{0.2971/\underline{109.5^\circ}}{0.0471/\underline{31.8^\circ}} \\ &= 6.3079/\underline{77.7^\circ} \Omega \end{aligned}$$

$$Y_2 = C = 0.0471/\underline{31.8^\circ} \text{ S}$$

$$\begin{aligned} Z_3 &= \frac{D-1}{C} = \frac{(1.116 + j0.2) - 1}{0.0471/\underline{31.8^\circ}} = \frac{0.2312/\underline{59.9^\circ}}{0.0471/\underline{31.8^\circ}} \\ &= 4.9087/\underline{28.1^\circ} \end{aligned}$$

$$\underline{4.17} \quad (a) \quad \gamma = \sqrt{YZ} = [(95/\underline{78^\circ})(0.001/\underline{90^\circ})]^{1/2} = 0.3082/\underline{84^\circ}$$

$$\gamma = \alpha + j\beta = 0.03221 + j0.30651$$

$$A = \cosh \gamma l = \cosh(\alpha + j\beta)l = \frac{1}{2} (e^{\alpha l/\underline{\beta l}} + e^{-\alpha l/\underline{\beta l}})$$

Thus,

$$A = \frac{1}{2} (e^{0.03221} \cdot e^{j0.30651} + e^{-0.03221} \cdot e^{-j0.30651})$$

$$= \frac{1}{2} (1.033/\underline{17.56^\circ} + 0.968/\underline{-17.56^\circ})$$

$$= 0.9539 + j0.0197 = 0.9541/\underline{1.18^\circ}$$

$$B = Z_c \sinh \gamma l = Z_c \sinh(\alpha + j\beta)l$$

$$= 93.5258/\underline{78.14^\circ} \Omega$$

$$C = Y_c \sinh \gamma l = \frac{\sinh \gamma l}{Z_c}$$

$$= 9.8448 \times 10^{-4}/\underline{90.14^\circ} \text{ S}$$

$$D = A = 0.9541/\underline{1.18^\circ}$$

Thus,

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} 0.9541/\underline{1.18}^\circ & 93.5258/\underline{78.14}^\circ \\ 9.8448 \times 10^{-4}/\underline{90.14}^\circ & 0.9541/\underline{1.18}^\circ \end{bmatrix}$$

(b) Using the T representation,

$$\frac{Z_T}{2} = \frac{A-1}{C} = 50.9203/\underline{66.72}^\circ \Omega$$

$$Y_T = C = 9.8448 \times 10^{-4}/\underline{90.14}^\circ \text{ S}$$

$$\begin{aligned} \begin{bmatrix} \bar{V}_S \\ \bar{I}_S \end{bmatrix} &= \begin{bmatrix} 1 + \frac{Z_T Y_T}{2} & Z_T \left(1 + \frac{Z_T Y_T}{4}\right) \\ Y_T & 1 + \frac{Z_T Y_T}{2} \end{bmatrix} \begin{bmatrix} \bar{V}_R \\ \bar{I}_R \end{bmatrix} \\ &= \begin{bmatrix} 0.9541/\underline{1.18}^\circ & 93.5258/\underline{78.14}^\circ \\ 9.8448 \times 10^{-4}/\underline{90.14}^\circ & 0.9541/\underline{1.18}^\circ \end{bmatrix} \begin{bmatrix} 79,674.34/\underline{0}^\circ \\ 241.18/\underline{-31.8}^\circ \end{bmatrix} \end{aligned}$$

Thus,

$$\bar{V}_{S(L-N)} = 93,303.697/\underline{11.05}^\circ \text{ V}$$

$$\bar{V}_{S(L-L)} = 161,606.7438/\underline{41.05}^\circ \text{ V}$$

$$(c) \bar{I}_S = 201.5953/\underline{-11.09}^\circ \text{ A}$$

$$(d) \phi_S = 11.05^\circ + 11.09^\circ = 22.14^\circ$$

$$(e) \cos \phi_S = 0.9263 \text{ lagging}$$

$$(f) \eta = 90.7\%$$

4.18 Using the π representation,

$$(a) \begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} 0.9541/\underline{1.18}^\circ & 93.5258/\underline{78.17}^\circ \\ 9.8448 \times 10^{-4}/\underline{90.14}^\circ & 0.9541/\underline{1.18}^\circ \end{bmatrix}$$

$$(b) \bar{V}_{S(L-L)} = 161,606.7438/\underline{41.05}^{\circ} \text{ V}$$

$$(c) \bar{I}_S = 201.5953/\underline{-11.09}^{\circ} \text{ A}$$

$$(d) \cos\phi_S = 0.9263 \text{ lagging}$$

$$(e) \eta = 90.7\%$$

4.19 Assuming a short line,

$$(a) \begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} 1 & 95/\underline{78}^{\circ} \\ 0 & 1 \end{bmatrix}$$

$$(b) \bar{V}_S = \bar{V}_R + \bar{I}_R \bar{Z}_L \\ = 79,674.34/\underline{0}^{\circ} + (241.18/\underline{-31.8}^{\circ})(95/\underline{78}^{\circ})$$

$$\bar{V}_{S(L-N)} = 97,001.0/\underline{9.84}^{\circ} \text{ V}$$

$$\bar{V}_{S(L-L)} = 168,010.6/\underline{30}^{\circ} + 9.84^{\circ} = 168,010.6/\underline{39.84}^{\circ} \text{ V}$$

$$(c) \bar{I} = \bar{I}_S = \bar{I}_R = 241.18/\underline{-31.8}^{\circ} \text{ A}$$

$$(d) \cos\phi_S = \cos(9.84^{\circ} + 31.8^{\circ}) = 0.7473 \text{ lagging}$$

$$(e) \eta = \frac{(138 \times 10^3)(0.85)}{(168,010.6)(0.7473)} 100 = 93.4\%$$

4.20 (a) $\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} 1 & 95/\underline{78}^{\circ} \\ 0 & 1 \end{bmatrix}$

$$(b) \bar{V}_{S(L-L)} = 168,010.6/\underline{39.84}^{\circ} \text{ V}$$

$$(c) \bar{I}_S = 241.18/\underline{-31.8}^{\circ} \text{ A}$$

$$(d) \cos\phi_S = 0.7473 \text{ lagging}$$

(e) $\eta = 93.4\%$

4.21 $z = 0.1858 + j120\pi(2.6 \times 10^{-3}) = 0.9977/\underline{79.27^\circ} \Omega/\text{mi}$

$y = j120\pi(0.012 \times 10^{-6}) = 4.5239 \times 10^{-6}/\underline{90^\circ} \text{ S}/\text{mi}$

Thus,

$Z = z\ell = (0.9977/\underline{79.27^\circ})75 = 74.828/\underline{79.27^\circ} \Omega$

$Y = y\ell = (4.5239 \times 10^{-6}/\underline{90^\circ})75 = 339.29 \times 10^{-6}/\underline{90^\circ} \text{ S}$

(a) Since the line has medium length,

$A = 1 + \frac{YZ}{2} = 987.53 \times 10^{-3}/\underline{0.14^\circ}$

$B = Z + \frac{YZ^2}{4} = 74.361/\underline{79.34^\circ}$

$C = Y = 339.29 \times 10^{-6}/\underline{90^\circ}$

$D = A = 987.53 \times 10^{-3}/\underline{0.14^\circ}$

(b)
$$\begin{bmatrix} \bar{V}_S \\ \bar{I}_S \end{bmatrix} = \begin{bmatrix} 987.53 \times 10^{-3}/\underline{0.14^\circ} & 74.361/\underline{79.34^\circ} \\ 339.29 \times 10^{-5}/\underline{90^\circ} & 987.53 \times 10^{-3}/\underline{0.14^\circ} \end{bmatrix} \begin{bmatrix} 79,674.34/\underline{0^\circ} \\ 209.18/\underline{-31.8^\circ} \end{bmatrix}$$

$$\bar{V}_{S(L-N)} = (987.53 \times 10^{-3}/\underline{0.14^\circ})(79,674.34/\underline{0^\circ}) + (74.361/\underline{79.34^\circ})(209.18/\underline{-31.8^\circ}) = 87,624.628/\underline{7.65^\circ}$$

$$\bar{V}_{S(L-L)} = 151,770.3077/\underline{30^\circ} + 7.65^\circ = 151,770.3077/\underline{37.65^\circ}$$

(c)
$$\begin{aligned} \bar{I}_S &= (339.29 \times 10^{-6}/\underline{90^\circ})(79,674.34/\underline{0^\circ}) + (987.53 \times 10^{-3}/\underline{0.14^\circ})(209.18/\underline{-31.8^\circ}) \\ &= 193.7538/\underline{-24.82^\circ} \text{ A} \end{aligned}$$

(d) $\cos\phi_S = \cos(7.65^\circ + 24.82^\circ) = \cos 32.47^\circ = 0.8437 \text{ lagging}$

$$(e) P_S = \sqrt{3} V_{S(L-L)} I_S \cos \phi_S$$

$$= \sqrt{3} (151,770.3077)(193.7538)(0.8437) = 42,971.4 \text{ kW}$$

$$(f) P_R = \sqrt{3} V_{R(L-L)} I_R \cos \phi_R$$

$$= \sqrt{3} (138 \times 10^3)(209.18)(0.85) = 42,499 \text{ kW}$$

$$\text{Thus, } P_{\text{LOSS}} = P_S - P_R = 472.4 \text{ kW}$$

$$(g) \eta = \frac{P_R}{P_S} \times 100 = 98.9\%$$

$$(h) \%V_{\text{Reg}} = \frac{87,624.628 - 79,674.34}{79,674.34} \times 100 = 9.98\%$$

$$(i) \bar{I}_c = \frac{\bar{Y}}{2} \bar{V}_{S(L-N)} = \left(\frac{j339.29 \times 10^{-6}}{2} \right) (87,624.628 / \underline{7.65}^\circ)$$

$$= 14.8651 / \underline{97.64}^\circ \text{ A}$$

$$(j) \bar{V}_{R(L-N)} = \bar{V}_{S(L-N)} - \bar{Z} \bar{I}_c$$

$$= 87,624.628 / \underline{7.65}^\circ - (74.828 / \underline{79.27}^\circ) (14.8651 / \underline{97.65}^\circ)$$

$$= 88,717.7469 / \underline{7.52}^\circ \text{ V}$$

$$\bar{V}_{R(L-L)} = 153,663.6452 / \underline{30}^\circ + \underline{7.92}^\circ = 153,663.6452 / \underline{37.52}^\circ$$

$$\underline{4.22} \quad \begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} 1 & 0 \\ Y & 1 \end{bmatrix} \begin{bmatrix} 1 & Z \\ 0 & 1 \end{bmatrix} = \begin{bmatrix} 1 & Z \\ Y & 1 + YZ \end{bmatrix}$$

$$\underline{4.23} \quad \begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} 1 & Z \\ 0 & 1 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ Y & 1 \end{bmatrix} = \begin{bmatrix} 1 + YZ & Z \\ Y & 1 \end{bmatrix}$$

4.24 Consider the series combination of two networks, as shown in Figure 2.43, the various voltages and currents being as shown.

$$V = A_2 V_R + B_2 I_R$$

$$I = C_2 V_R + D_2 I_R$$

$$\begin{aligned} V_R &= A_1 (A_2 V_R + B_2 I_R) + B_1 (C_2 V_R + D_2 I_R) \\ &= (A_1 A_2 + B_1 C_2) V_R + (A_1 B_2 + B_1 D_2) I_R \end{aligned}$$

$$\begin{aligned} I_R &= C_1 V + D_1 I \\ &= C_1 (A_2 V_R + B_2 I_R) + D_1 (C_2 V_R + D_2 I_R) \\ &= (C_1 A_2 + D_1 C_2) V_R + (C_1 B_2 + D_1 D_2) I_R \end{aligned}$$

Therefore, the equivalent A, B, C, D constants for two networks connected in series are

$$A = A_1 A_2 + B_1 C_2 \quad B = A_1 B_2 + B_1 D_2$$

$$C = C_1 A_2 + D_1 C_2 \quad D = C_1 B_2 + D_1 D_2$$

4.25

If the two networks are connected in parallel, as shown in Figure 2.45,

$$V_S = A_1 V_R + B_1 I_{R1} = A_2 V_R + B_2 I_{R2}$$

$$I_{S1} = C_1 V_R + D_1 I_{R1}$$

$$I_{S2} = C_2 V_R + D_2 I_{R2}$$

$$I_{R1} = \frac{V_S - A_1 V_R}{B_1}$$

$$I_{R2} = \frac{V_S - A_2 V_R}{B_2}$$

$$I_R = I_{R1} + I_{R2}$$

$$V_S = A_1 V_R + B_1 (I_R - I_{R2})$$

$$= A_1 V_R + B_1 \left[I_R - \frac{V_S - A_2 V_R}{B_2} \right]$$

$$= \frac{A_1 B_2 + A_2 B_1}{B_1 + B_2} V_R + \frac{B_1 B_2}{B_1 + B_2} I_R$$

$$I_S = I_{S1} + I_{S2}$$

$$= (C_1 + C_2) V_R + D_1 I_{R1} + D_2 (I_R - I_{R1})$$

$$= (C_1 + C_2) V_R + \frac{(D_1 - D_2)(V_S - A_1 V_R)}{B_1} + D_2 I_R$$

Substituting for V_S and collecting terms,

$$I_S = [C_1 + C_2 + \frac{(A_1 - A_2)(D_2 - D_1)}{B_1 + B_2}] V_R + [\frac{D_1 B_2 + D_2 B_1}{B_1 + B_2}] I_R$$

therefore,

$$A = \frac{A_1 B_2 + A_2 B_1}{B_1 + B_2}$$

$$B = \frac{B_1 B_2}{B_1 + B_2}$$

$$C = C_1 + C_2 + \frac{(A_1 - A_2)(D_2 - D_1)}{B_1 + B_2}$$

$$D = \frac{D_1 B_2 + D_2 B_1}{B_1 + B_2}$$

4.26 From Example 2.8,

$$z = \frac{Z}{52} = \frac{95/\underline{78}^\circ}{52} = 1.8269/\underline{78}^\circ \Omega/\text{mi}$$

$$y = \frac{Y}{52} = \frac{0.001/\underline{90}^\circ}{52} = 1.9231 \times 10^{-5}/\underline{90}^\circ \text{ S}/\text{mi}$$

$$(a) \quad \gamma = \sqrt{yz} = 5.927319 \times 10^{-3}/\underline{84}^\circ$$

$$= 6.19574 \times 10^{-4} + j5.894851 \times 10^{-3}$$

Thus, $\alpha = 6.19574 \times 10^{-4}$ nepers/mi

$$\beta = 5.894851 \times 10^{-3} \text{ radians/mi}$$

$$(b) \lambda = \frac{2\pi}{\beta} = \frac{2\pi}{5.894851 \times 10^{-3}} = 1,065.8769 \text{ mi}$$

$$\mathcal{V} = \lambda f = 1,065.8769 \times 60 = 63,952.615 \text{ mi/s}$$

$$(c) \bar{I}_R = \frac{49 \times 10^6}{\sqrt{3} (138 \times 10^3)(0.85)} / \underline{-31.79^\circ} = 241.1779 / \underline{-31.79^\circ} \text{ A}$$

$$\bar{Z}_c = \left(\frac{Z}{Y}\right)^{1/2} = 308.2169 / \underline{-6^\circ} \Omega$$

$$\bar{V}_{R(\text{incident})} = \frac{\bar{V}_R + \bar{I}_R \bar{Z}_c}{2} = 72,860.71 / \underline{-18.21^\circ} \text{ V}$$

$$\bar{V}_{R(\text{reflected})} = \frac{\bar{V}_R - \bar{I}_R \bar{Z}_c}{2} = 25,063.13 / \underline{65.32^\circ} \text{ V}$$

$$(d) \bar{V}_{R(L-N)} = \bar{V}_{R(\text{incident})} + \bar{V}_{R(\text{reflected})} = 79,674.33 / \underline{0^\circ}$$

$$V_{R(L-L)} = \sqrt{3} V_{R(L-N)} = 138,000 \text{ V}$$

$$(e) \bar{V}_{S(\text{incident})} = \frac{\bar{V}_R + \bar{I}_R \bar{Z}_c}{2} e^{j\ell}$$

$$\text{where } j\ell = 1.18546 / \underline{84^\circ}$$

$$= 123.915 \times 10^{-3} + j1.17897$$

$$\bar{V}_{S(\text{incident})} = (72,860.71 / \underline{-18.21^\circ}) (e^{123.915 \times 10^{-3} + j1.17897})$$

$$= 82,472.5 / \underline{49.34^\circ} \text{ V}$$

$$\bar{V}_{S(\text{reflected})} = (25,063.13 / \underline{65.32^\circ}) (e^{-123.915 \times 10^{-3} - j1.17897})$$

$$= 22,142.2 / \underline{-2.23^\circ} \text{ V}$$

$$\begin{aligned}
 \text{(f)} \quad \bar{V}_{S(L-N)} &= \bar{V}_{S(\text{incident})} + \bar{V}_{S(\text{reflected})} \\
 &= 97,787.4 / \underline{39.12}^\circ \text{ V}
 \end{aligned}$$

$$V_{S(L-L)} = \sqrt{3} V_{S(L-N)} = 169,373 \text{ V}$$

4.27 From Prob. 2.37, $\bar{Z}_c = 308.2169 / \underline{-6}^\circ \Omega$

$$\text{SIL} \approx \frac{138^2}{308.2169} = 61.7877 \text{ MW}$$

4.28 (a) Since the distributed reactance of the line has not been altered, Z_c and SIL of the line are the same as in Example 2.17.

$$\text{(b)} \quad X_{L(\text{new})} = 0.40 X_{L(\text{old})} = 0.40 \times 117.6 = 47.04 \Omega/\phi$$

$$\begin{aligned}
 \text{Thus, } P_{\max} &= \frac{V_S R_R}{X_L} = \frac{(345 \times 103)^2}{47.04} \\
 &= 2530.3 \text{ MW}/3\phi
 \end{aligned}$$

4.29 (a) $2 \times \text{SIL} = 2 \times 416.5 = 833 \text{ MVA}/3\phi/\text{mi}$

$$X_L = 0.60 X_{L(\text{old})} = 0.60 \times 117.6 = 70.56 \Omega/\phi$$

$$\text{Therefore, } I = \frac{833 \times 10^6}{\sqrt{3} (345 \times 10^3)} = 1394 \text{ A}$$

$$V_c = I X_c = 1394 \times 70.56 = 98,360.64 \text{ V}$$

Since series connection builds up the voltage rating and parallel connection builds up the current rating,

$$\begin{aligned}\text{No. of series capacitors} &= \frac{V_c}{12,000} = \frac{98,360.64}{12,000} \\ &= 8.2 \text{ or } 9/\Phi\end{aligned}$$

$$\text{No. of parallel capacitors} = \frac{1394}{12.5} = 111.5 \text{ or } 112/\Phi$$

36.

Since each capacitor can stand for 12 kV and (150 kvar/12 kV) = 12.5 A. Therefore, the numbers of series- and parallel-connected capacitors are 9 and 112, respectively. Thus, the total number of capacitors required is $9 \times 112 = 1008$ per phase or 3024 per three phase.

(b) Therefore,

$$I_{\text{actual}} = 112(12.5\text{A}) = 1400 \text{ A} > 1304 \text{ A}$$

$$V_{\text{actual}} = 9(12 \text{ kV}) = 108 \text{ kV} > 98,360.64 \text{ V}$$

$$\text{Thus, } Q_c = VI = (108 \text{ kV})(1400) = 151,200 \text{ kvar}/\Phi$$

$$\text{Cost of capacitor bank} = (151,200 \text{ kvar})(\$1.50/\text{kvar})$$

$$= \$226,800/\Phi$$

$$= \$680,400/3\Phi$$

4.30 (a) From Table 2.6, $y = 1.08 \times 10^{-4}/89.7^\circ \text{ S/mi}$

$$\text{thus, } b = y \sin 89.7^\circ = (1.08 \times 10^{-4})(1.0) = 1.08 \times 10^{-4} \text{ S/mi}$$

Alternatively, the charging current is

$$i_c = bV_{\text{an}}$$

$$\text{from which, } b = \frac{i_c}{V_{\text{an}}} = \frac{21.6 \times \sqrt{3}}{345,000} = 1.08 \times 10^{-4} \text{ S/mi}$$

(b) Since $I_{\ell_o} = I_T$,

$$\ell_o = \frac{I_{\ell_o}}{V_s b} = \frac{585 \times \sqrt{3}}{(345,000)(1.08 \times 10^{-4})} = 27.194 \text{ mi}$$

for cable ampacity of 585 A. Note that it is given as 27.1 mi in Table 2.6.

4.31

$$\bar{I}_{l_0} = \frac{\bar{V}_S}{\bar{Z}_c} \tanh \bar{Y} l_0$$

$$\tanh \bar{Y} l_0 = \tanh[0.179/\underline{83.9^\circ}]$$

$$= \frac{0.179 \cos 83.9^\circ + j0.179 \sin 83.9^\circ + 0.000956 \cos 251.7^\circ + j0.000956 \sin 251.7^\circ}{1 + 0.016 \cos 167.8^\circ + j0.016 \sin 167.8^\circ + j0.000956 \sin 251.7^\circ}$$

$$= 0.181/\underline{83.75^\circ}$$

Therefore,

$$\bar{I}_{l_0} = \left[\frac{345 \times 10^3 / 0^\circ}{\sqrt{3} (61.2 / \underline{-5.9^\circ})} \right] [0.181 / \underline{83.75^\circ}]$$

$$= 590 / \underline{89.65^\circ} \text{ A}$$

Note that it is given in Table 2.6 as

$$I_{l_0} = I_T = 585 \text{ A}$$

4.32

$$P_R = \frac{V_S \cdot V_R}{Z} \cos(\theta - \delta) - \frac{V_R^2}{Z} \cos \theta$$

$$\text{If } \theta = 90, \sin \delta \triangleq \cos(90^\circ - \delta) \triangleq \sin(180 - \delta)$$

$$\text{and } \cos \theta = 0.$$

Therefore,

$$P_{R, \max} = \frac{V_S V_R}{Z} \cos(90^\circ - \delta) = \frac{V_S V_R}{Z} \sin \delta$$

$$\text{If } R = 0: Z = X$$

$$P_{R,\max} = \frac{|V_S| |V_R|}{X} \sin \delta$$

4.33 Since, $\bar{S} = \bar{V}\bar{I}^*$ and

$$\bar{I} = \frac{\bar{V}_S - \bar{V}_R}{\bar{Z}} = \frac{V_S/\underline{\theta} - 115 \times 10^3/\underline{0}^\circ}{15/\underline{90}^\circ}$$

$$\frac{19.22 \times 10^6/\underline{38.66}^\circ}{V_S/\underline{\theta}} = \frac{(V_S/\underline{\theta}) \left(\frac{V_S/\underline{\theta} - 115 \times 10^3/\underline{0}^\circ}{15/\underline{-90}^\circ} \right)}{V_S/\underline{\theta}}$$

and by multiplying both sides by $15/\underline{-90}^\circ$

$$\frac{288 \times 10^6/\underline{-51.34}^\circ - \theta}{V_S} + 115 \times 10^3/\underline{0}^\circ = V_S/\underline{-\theta}$$

$$V_S/\underline{\theta} = 115 \times 10^3/\underline{0}^\circ + \frac{288 \times 10^6/\underline{51.34}^\circ + \theta}{V_S}$$

By using the trial and error method,

$$\bar{V}_S \approx 116,517/\underline{0.96}^\circ \text{ V}$$

Alternatively, since $R = 0$, i.e., $Z = 0 + j15 \Omega$ there are no losses.

$$\bar{S} = P + jQ = 15 + j12 = 19.2094/\underline{38.66}^\circ \text{ MVA}$$

therefore, $|\bar{S}| = 19.2094 \text{ MVA}$

$$I_R = \frac{19.2094 \times 10^6}{115 \times 10^3} = 167.038 \text{ A}$$

$$\bar{I}_R = 167.038/\underline{-38.66}^\circ \text{ A}$$

Using \bar{V}_R as the reference,

$$\begin{aligned}
 \bar{V}_S &= \bar{V}_R + \bar{I}_R \bar{Z}_L \\
 &= 115 \times 10^3 + (167.038 / \underline{-38.66^\circ})(15 / \underline{90^\circ}) \\
 &= 116,581.64 / \underline{0.96^\circ} \text{ A}
 \end{aligned}$$

$$\begin{aligned}
 \text{(b) } \bar{I}_S &= \frac{\bar{V}_S - \bar{V}_R}{\bar{Z}} \\
 &= \frac{116,517 / \underline{0.96^\circ} - 115 / \underline{0^\circ}}{15 / \underline{90^\circ}} = 164.78 / \underline{-37.39^\circ} \text{ A}
 \end{aligned}$$

Alternatively,

$$\begin{aligned}
 \bar{S}_S &= \bar{V}_S \bar{I}_S^* \\
 \bar{I}_S^* &= \frac{(15 + j12) \times 10^6}{116,581.64 / \underline{0.96^\circ}} = 164.7719 / \underline{37.7^\circ}
 \end{aligned}$$

$$\text{Therefore, } \bar{I}_S = 164.7719 / \underline{-37.7^\circ} \text{ A}$$

4.34 (a) $D = (D_{ab} \times D_{bc} \times D_{ca})^{1/3} = (10 \times 8 \times 18)^{1/3} = 11,292 \text{ ft}$

From Table A.1, $X_a = 0.422 \text{ } \Omega/\text{mi}$

From Table A.8, $X_d = 0.2941 \text{ } \Omega/\text{mi}$

Therefore, $X_L = X_a + X_d = 0.422 + 0.2941 = 0.7161 \text{ } \Omega/\text{mi}$

(b) From Table A.1, $X'_a = 0.0954 \text{ M}\Omega - \text{mi}$

From Table A.10, $X'_d = 0.0718 \text{ M}\Omega - \text{mi}$

Thus, $X_c = X'_a + X'_d = 0.0954 + 0.0718 = 0.1672 \text{ M}\Omega - \text{mi}$

(c) From Table A.1, $r = 0.0871 \text{ } \Omega/\text{mi}$. Therefore,

$$R = r \times \ell = 0.0871 \times 100 = 8.71 \text{ } \Omega$$

$$(d) X_L = 0.7161 \times 100 = 71.61 \Omega$$

$$(e) X_C = \frac{0.1672}{100} = 1.672 \text{ k}\Omega$$

$$\underline{4.35} (a) \gamma = \sqrt{yz} = [(0.7688/\underline{77.4}^\circ)(4.5239 \times 10^{-6}/\underline{90}^\circ)]^{1/2}$$

$$= [0.7688 \times 4.5239 \times 10^{-6}]^{1/2} / \frac{77.4^\circ + 90^\circ}{2}$$

$$= 0.0019/\underline{83.7}^\circ = 0.0002 + j0.0019$$

$$(b) \text{ Thus, } \alpha = 0.0002 \text{ nepers/mi and } \beta = 0.0019 \text{ rad/mi}$$

$$(c) Z_c = \left(\frac{z}{y}\right)^{1/2} = \left(\frac{0.7688}{4.5239 \times 10^{-6}}\right)^{1/2} / \frac{77.4^\circ - 90^\circ}{2}$$

$$= 412.24/\underline{-6.3}^\circ \Omega$$

$$(d) \text{ SIL} = \frac{(138 \times 10^3)^2}{412.24} = 46.1964 \text{ MW}$$

$$(e) I_R = \frac{50 \times 10^6}{\sqrt{3} \times 138 \times 10^3} = 209.4 \text{ A or } \bar{I}_R = 209.4/\underline{-31.8}^\circ \text{ A}$$

$$(f) \bar{V}_{S(\text{incident})} = \frac{\bar{V}_R + \bar{I}_R \bar{Z}_c}{2} e^{\alpha l} \cdot e^{j\beta l}$$

$$= (78,505.1/\underline{-19.8}^\circ) e^{0.0307} \cdot e^{j0.278}$$

$$= (78,505.1/\underline{-19.8}^\circ)(1.0312/\underline{15.9}^\circ)$$

$$= 80,954.5/\underline{-3.9}^\circ \text{ V}$$

$$\text{where } (0.278 \text{ rad})(57.3^\circ/\text{rad}) = 15.9^\circ$$

$$(g) \bar{V}_{S(\text{reflected})} = \frac{\bar{V}_R - \bar{I}_R \bar{Z}_c}{2} e^{-\alpha l} \cdot e^{-j\beta l}$$

$$= (27,282/\underline{77.5}^\circ)(0.9698/\underline{-15.9}^\circ)$$

$$= 26,458.1/\underline{6.6}^\circ \text{ V}$$

4.36 (a)
$$\bar{V}_{R(\text{incident})} = \frac{\bar{V}_R + \bar{I}_R \bar{Z}_c}{2}$$

$$= \frac{79,674/\underline{0}^\circ + (209.18/\underline{-31.8}^\circ)(469.12/\underline{-5.37}^\circ)}{2}$$

$$= 84,367.77/\underline{-20.59}^\circ \text{ V}$$

$$\bar{V}_{R(\text{reflected})} = \frac{\bar{V}_R - \bar{I}_R \bar{Z}_c}{2} = 29,684.15/\underline{88.65}^\circ \text{ V}$$

(b)
$$e^{j\beta \ell} = e^{j0.3202} = (0.3202 \text{ rad})(57.3^\circ/\text{rad}) = 18.35^\circ$$

$$\bar{V}_{S(\text{incident})} = \frac{\bar{V}_R + \bar{I}_R \bar{Z}_c}{2} e^{\alpha \ell} \cdot e^{j\beta \ell}$$

$$= (84,366.77/\underline{-20.59}^\circ) e^{0.0301} / \underline{18.35}^\circ$$

$$= 86,946/\underline{-2.24}^\circ \text{ V}$$

$$\bar{V}_{S(\text{reflected})} = \frac{\bar{V}_R - \bar{I}_R \bar{Z}_c}{2} e^{-\alpha \ell} \cdot e^{-j\beta \ell}$$

$$= (29,684.15/\underline{88.65}^\circ) e^{-0.0301} / \underline{-18.35}^\circ$$

$$= 28,802.5/\underline{70.3}^\circ \text{ V}$$

(c)
$$\bar{V}_{S(L-N)} = \bar{V}_{S(\text{incident})} + \bar{V}_{S(\text{reflected})} = 99,458.1/\underline{13.8}^\circ \text{ V}$$

Thus, $|V_{S(L-L)}| = \sqrt{3} V_{S(L-N)} = 172,266.5 \text{ V}$

4.37 (a) From Table A.3, $D_s = 0.0493 \text{ ft}$, therefore

$$D_s^b = (D_s \times d)^{1/2} = (0.0493 \times 0.3048 \times 12 \times 0.0254)^{1/2} = 0.0677 \text{ m}$$

$$D_{eq} = (D_{12} \cdot D_{23} \cdot D_{31})^{1/3} = (25 \times 25 \times 50 \times 0.3048^3)^{1/3} = 9.6006 \text{ m}$$

$$L_a = 2 \times 10^{-7} \ln \frac{D_{eq}}{D_s^b} = 2 \times 10^{-7} \ln \frac{9.606}{0.0677} = 0.9909 \mu\text{H/m}$$

$$(b) X_L = 2\pi f L_a = 2\pi 60 \times 0.9909 \times 10^{-6} \times 10^3 = 0.3736 \Omega/\text{km}$$

$$X_L = 0.3736 \times 1.609 = 0.6011 \Omega/\text{mi}$$

$$(c) Z_B = \frac{345^2}{100} = 1190.25 \Omega$$

$$X_L = \frac{0.3736 \times 200}{1190.25} = 0.0628 \text{ pu}$$

(d) From Table A.3, the outside diameter of the subconductor is 1.465 in, therefore its radius is

$$r = \frac{1.465 \times 0.3048}{2 \times 12} = 0.0186 \text{ m}$$

$$D_{sc}^b = (rd)^{1/2} = (0.0186 \times 12 \times 0.0254)^{1/2} = 0.0753 \text{ m}$$

Thus, the line-to-neutral capacitance of the line is

$$C_n = \frac{55.63 \times 10^{-12}}{\ln \frac{D_{eq}}{D_{sc}^b}} = \frac{55.63 \times 10^{-12}}{\ln \frac{9.606}{0.0753}} = 11.473 \times 10^{-12} \text{ F/m}$$

$$(e) X_c = \frac{1}{2\pi f C_n} = \frac{10^{12} \times 10^{-3}}{2\pi 60 \times 11.473} = 0.231 \times 10^6 \Omega\text{-km}/\Phi$$

$$X_c = \frac{0.231 \times 10^6}{1.609} = 0.14369 \times 10^6 \Omega\text{-mi}/\Phi$$