

2 Problem solutions

1.3.

The total inertia at motor shaft J_t (1.13) is

$$J_t = J_m + J_L a^2 = 0.02 + 2 \cdot 1/100 = 0.04 \text{ Kgm}^2$$

The motor torque requirement (1.11) is

$$T_e = J_t \dot{\Omega} + T_L = 0.04 \cdot 1884 + 200 = 275.36 \text{ Nm for } 0 \leq t \leq 0.2 \text{ s}$$

$$T_e = T_L = 200 \text{ Nm for } 0.2 \leq t \leq 0.8 \text{ s}$$

$$T_e = -J_t \dot{\Omega} + T_L = -0.04 \cdot 1884 + 200 = 124.64 \text{ Nm for } 0.8 \leq t \leq 1 \text{ s}$$

1.4.

The motor base torque T_{eb} is

$$T_{eb} = \frac{P_b}{(\omega_b / p)} = \frac{100 \cdot 10^3}{367/2} \approx 545 \text{ Nm}$$

For same power at $\omega_{\max} = 3\omega_b$, T_e is

$$T_e = T_{eb} \frac{\omega_b}{\omega_{\max}} = \frac{T_{eb}}{3} = \frac{545}{3} = 148.33 \text{ Nm}$$


With zero losses the generator torque at $(-P_b)$ is simply

$$T_e = -T_{eb} = -545 \text{ Nm at } \omega_b \text{ (base speed)}$$


CHAPTER 3

3.1.

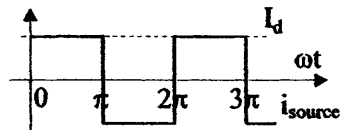- a. As seen on Figure 3.12, also, for constant d.c. current I_d the source current will change stepwise from $-I_d$ to I_d at $\omega t = 0$ and from $+I_d$ to $-I_d$ at $\omega t = \pi$.



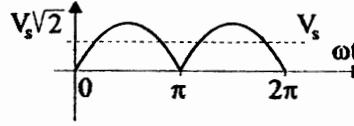- b. The d.c. voltage will look as in the figure below



The average output voltage $V_{av} = \frac{2}{\pi} \sqrt{2} V_s = \frac{2}{\pi} \sqrt{2} \cdot 120 = 107.77 \text{ V}$.

c. The source current fundamental (rms) I_{s1} is

$$I_{s1} = \frac{4I_d}{\pi\sqrt{2}} = 50 \frac{4}{\pi\sqrt{2}} = 45.17 \text{ A}$$

The displacement power factor DPF is (3.6)

$$\text{DPF} = \cos \phi_1 = 1$$

as the source current fundamental and voltage are in phase.

The power factor PF (3.10) is

$$\text{PF} = \frac{I_{s1}}{I_s} \text{DPF} = \frac{I_{s1}}{I_s}$$

I_s , (3.11), is

$$I_s = \sqrt{I_{s1}^2 + \sum_{v=2}^{\infty} I_{sv}^2} = I_{s1} \sqrt{1 + \frac{1}{3^2} + \frac{1}{5^2} + \frac{1}{7^2} + \dots} \approx 1.0918$$


$$I_{sv} = \frac{4I_d}{v\pi\sqrt{2}} = \frac{I_{s1}}{v}$$

Finally

$$\text{PF} = \frac{I_{s1}}{I_{s1} \cdot 1.0918} = 0.916$$

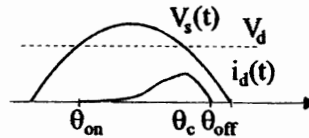3.2.

The current waveform follows from figure below (Figure 3.9).



The turn on angle θ_{on} is obtained when $V_d = V_s(t)$: $120 = 120\sqrt{2} \sin \theta_{on}$.
Thus $\theta_{on} = 45^\circ$, $\theta_c = 135^\circ$ (at θ_c the current is maximum).

The turn off angle θ_{off} is obtained by making zero the average voltage on the source inductance (3.17).

4 Problem solutions

$$\int_{\theta_{on}}^{\theta_{off}} (V_s \sqrt{2} \sin \omega t - V_d) d(\omega t) = 0$$

or
$$V_s \sqrt{2} (\cos \theta_{on} - \cos \theta_{off}) - V_d (\theta_{off} - \theta_{on}) = 0$$

$$\sqrt{2} (1/\sqrt{2} - \cos \theta_{off}) = \theta_{off} - \theta_{on}$$

Approximately $\theta_{off} \approx 171^\circ$ and thus (3.20)

$$i_d = 0 \text{ for } 0 < \theta < 45^\circ \text{ and } 171^\circ < \theta < 180^\circ$$

and
$$i_d = \frac{V_s \sqrt{2} (\cos \theta_{on} - \cos \omega t) - V_d (\omega t - \theta_{on})}{\omega L_s}$$

$$= \frac{120 [\sqrt{2} (0.707 - \cos \omega t) - (\omega t - \pi/4)]}{367 \cdot 5 \cdot 10^{-3}} \text{ for } 45^\circ < \theta < 171^\circ$$

3.3.

The maximum overlapping angle $u_{max} = 30^\circ$ is (from 3.28)

$$\cos u_{max} = 1 - \frac{2\omega L_s}{V_s \sqrt{2}} I_{dmax}$$

$$I_{dmax} = \frac{(1 - 0.867) 120 \sqrt{2}}{2 \cdot 367 \cdot 1 \cdot 10^{-3}} = 30.66 \text{ A}$$

The ideal d.c. voltage V_{d0} , (3.29), is

$$V_{d0} = \frac{2\sqrt{2}}{\pi} V_s = \frac{2\sqrt{2}}{\pi} 120 = 108 \text{ V}$$

While the actual one, V_d , (3.30), is

$$V_d = V_{d0} - \frac{2\omega L_s}{\pi} I_d = 108 - \frac{2 \cdot 367 \cdot 1 \cdot 10^{-3}}{\pi} \cdot 30.66 = 100.833 \text{ V}$$

CHAPTER 4

4.1.

- a. As the armature resistance $R_a = 0.14\Omega$ from (4.18) the voltage at standstill V_a for rated current is

$$V_a = R_a I_a = 0.14 \cdot 29.18 = 4.088 \text{ V}$$