

# Experiment

# 1

## Operational Amplifiers

### Experiment Questions

1. analog
2. linear
3. greater
4. 6, -
5. -5V

INPUTS		$V_{OUT}$ (V)
$V_1$	$V_2$	
+4	+1	-5
+2	+3	+5
+1	0	-5
+4	+4	0
0	+1	+5
+3	+2	-5

Figure 1-2 b

$V_{IN}$ (V)	$V_{OUT}$ (V)
+0.2	-1
-0.4	+2
0	0
+0.32	-1.6

Figure 1-3 b

$V_{IN}$ (V)	$V_{OUT}$ (V)
+0.3	-0.75
-0.15	+0.38
-2.0	-5
+0.4	-1

Figure 1-3 c

Input Voltage			Output Voltage	
$V_1$	$V_2$	$V_3$	Measured	Calculated
+1	+1	+1	-3	-3
+1	-1	-1	+1	+1
+2	-1	-1	0	0
-3	-1	+3	+1	+1
+1	+2	-1	-2	-2

Figure 1-4 b

## Schmitt Trigger

### Procedure Question Answer

1. No. Because the 7476 J-K flip-flop is negative-edge triggered, and reacts only to positive-to-negative-going signals that change abruptly. The rectified sine wave does not change fast enough.

### Step 5

Point 1
$V_{th-} = \underline{.9} \text{ VDC}$
$V_{th+} = \underline{1.7} \text{ VDC}$

Table 2-1

### Step 7





Waveform	At Point 1	At Point 2	Is the Flip-Flop Toggling (Yes, No)
Circuit (a)			NO
Circuit (b)			YES

Table 2-2

### Experiment Questions

1. - Convert electronic signals to square waves.  
- Perform NAND gate and Inverter logic functions.
2. D
3. edge
4. Low, High
5. hysteresis
6. Because when sine waves are counted, they must be converted to square waves before being applied to a flip-flop.

# Experiment 3

## Magnitude Comparator

### Procedure Question Answer

1. If the high-order bits are equal, then the output state is determined by comparing the low-order bits.

### Step 2A

Input B				Input A				Outputs		
B <sub>3</sub>	B <sub>2</sub>	B <sub>1</sub>	B <sub>0</sub>	A <sub>3</sub>	A <sub>2</sub>	A <sub>1</sub>	A <sub>0</sub>	A<B	A=B	A>B
0	0	0	0	0	0	0	0	0	1	0
0	1	0	0	0	0	0	1	1	0	0
1	0	0	1	1	0	0	0	1	0	0
0	0	1	1	0	1	0	0	0	0	1
0	0	0	1	1	0	0	1	0	0	1

Table 3-2

### Step 3B

Input B				Input A				Expansion Inputs			Outputs		
B <sub>3</sub>	B <sub>2</sub>	B <sub>1</sub>	B <sub>0</sub>	A <sub>3</sub>	A <sub>2</sub>	A <sub>1</sub>	A <sub>0</sub>	I <sub>A</sub> <B	I <sub>A</sub> =B	I <sub>A</sub> >B	A<B	A=B	A>B
0	0	0	0	1	1	1	1	1	0	0	0	0	1
0	0	0	1	0	0	0	1	0	0	1	0	0	1
0	1	1	0	0	1	1	0	0	1	0	0	1	0
1	1	1	0	1	1	0	1	0	0	1	1	0	0
0	1	0	1	1	1	1	0	0	1	0	0	0	1

Table 3-4

### Experiment Questions

1. 1111
2. Yes. By connecting a Low to the MSB of inputs A and B, and applying the three binary bits to the remaining inputs.
3.  $I_A > B = 0$   
 $I_A = B = 0$   
 $I_A < B = 1$
4. 4
5. When A is greater than B, or B is greater than A, the circuit would operate normally. When A is equal to B, however, output A<B would incorrectly go High—instead of output A=B.